



Analog IC Design

Lab 09 (Mini Project 01) Two-Stage Miller OTA

Part 1: gm/ID Design Charts

1) For $L = 0.28\mu$

PMOS:

 


Figure 1: intrinsic gain

 


Figure 2: ID/W

Lab 09 (Mini Project 01) Two-Stage Miller OTA

 


Figure 5:GM/CGG

 


Figure 4:VGS

NMOS

 


Figure 3: intrinsic gain

Lab 09 (Mini Project 01) Two-Stage Miller OTA

 


Figure 8:ID/W

 


Figure 7:GM/CGG

 


Figure 6:VGS

Lab 09 (Mini Project 01) Two-Stage Miller OTA



For $L=0.4\mu:0.4\mu:2\mu$

PMOS:

 


Figure 9:intrinsic gain

 


Figure 10:ID/W

Lab 09 (Mini Project 01) Two-Stage Miller OTA

 


Figure 12:GM/CGG

 


Figure 11:VGS

NMOS:

 


Figure 13: intrinsic gain

Lab 09 (Mini Project 01) Two-Stage Miller OTA

 


Figure 16: id/w

 


Figure 15: GM/CGG

 


Figure 14: VGS



Part 2: OTA Design :

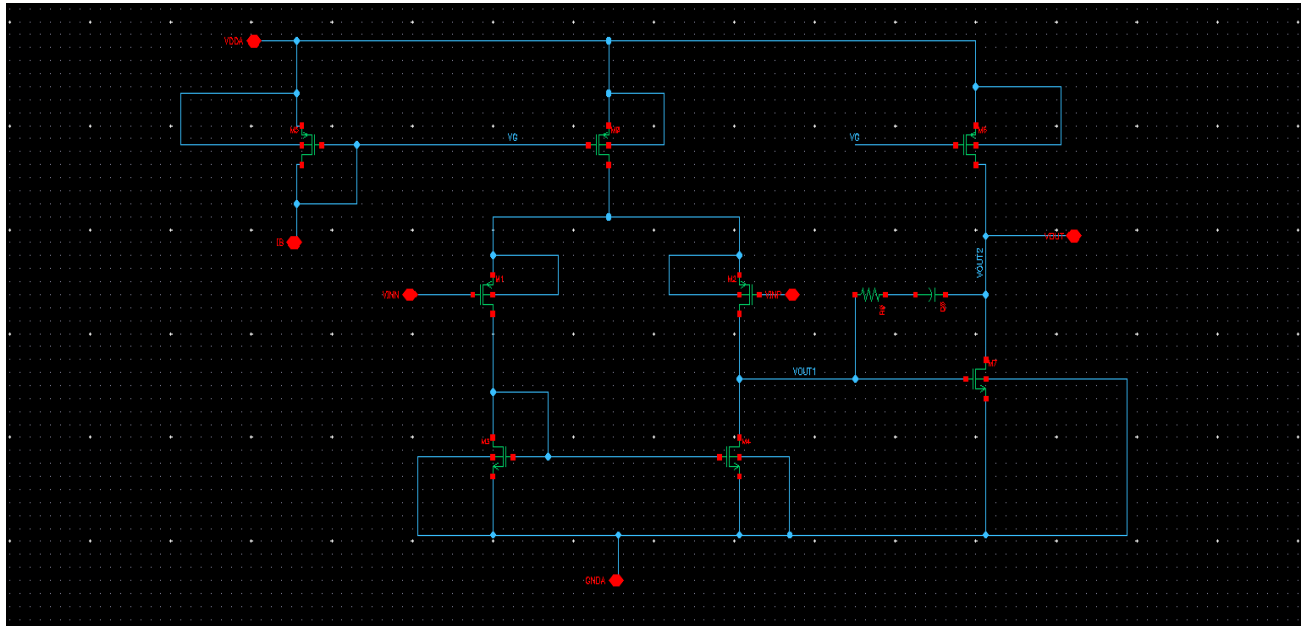


Figure 17: schematic

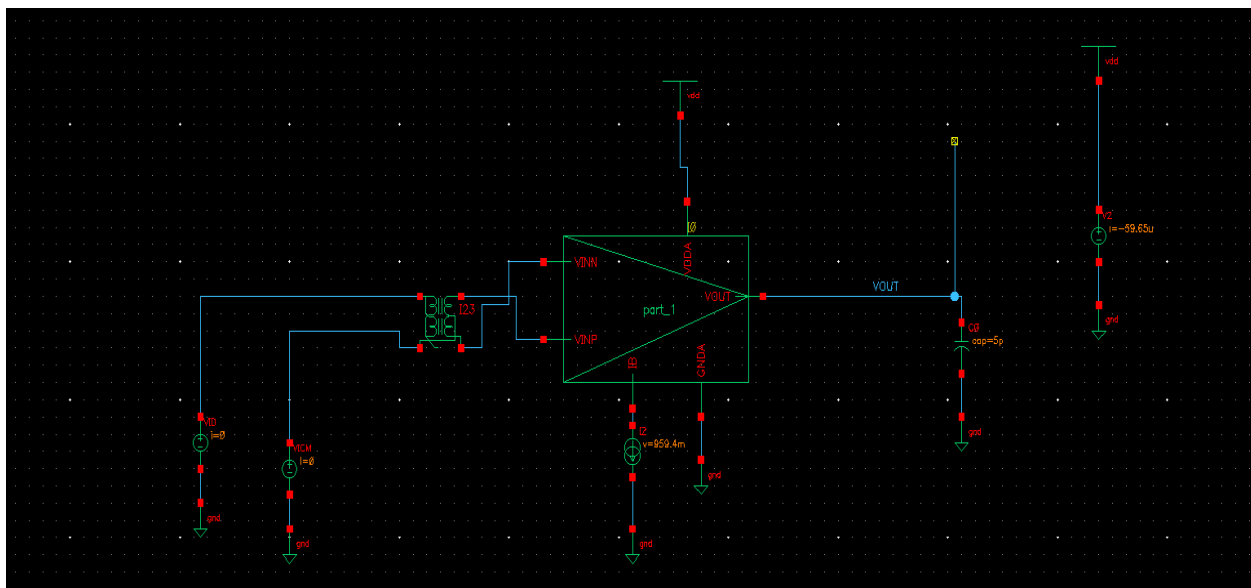


Figure 18: schematic with symbol

Lab 09 (Mini Project 01) Two-Stage Miller OTA



Design for input pair (PMOS):

PMOS input pair naturally supports low-end CMIR (towards GND)

Static gain error $\leq 0.05\%$ $\longrightarrow A_{OL} \leq 2000$ (for 2 stages)

So assume $A_{OL(1st\ stage)} = 64$, $A_{OL(2nd\ stage)} = 32$, Assume $i_{dM1} = 5u$, $i_{dM6} = 40u$

$CC=2p$, $t_{rise} = 2.2\tau$ $\longrightarrow GBW = \frac{1}{2\pi\tau} = 5\text{ MHz}$

$gm_{1,2} = 2\pi \times GBW \times CC = 62.83u$ $\longrightarrow \frac{gm_{1,2}}{i_{dM1}} = 12.57$

≈ 14 (for some margin)

$0.5 \times \frac{gm_{1,2}}{g_{ds}} = 64$

And from SA :

$L=425.8n \approx 440n$ (for some margin)

$W = 8.91u$, $V_{SG}=862.1mV$,

$v_{thp}=781.6mV$ $r_{on}=2M\Omega$

We assign larger gain to stage-1 because it:

reduces input-referred offset & noise, and leaves stage-2 mainly for providing swing & driving CL.

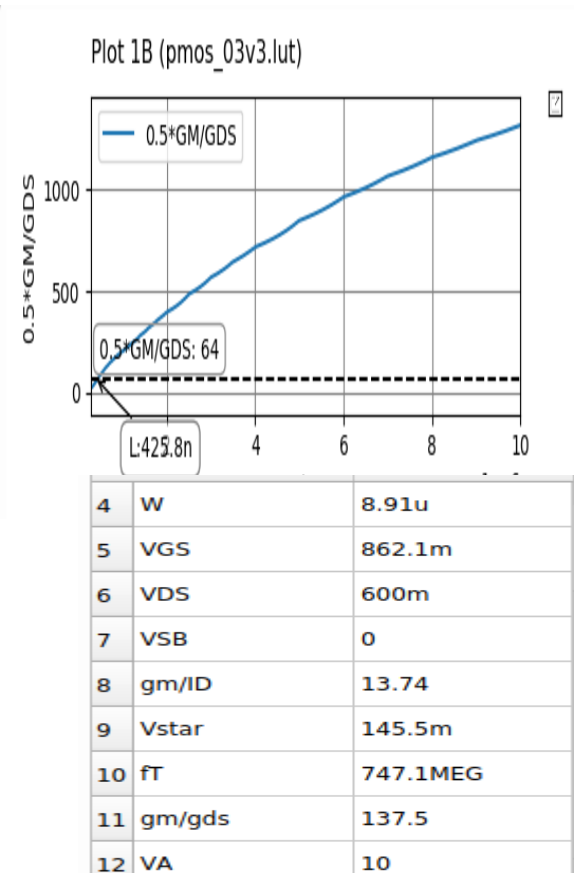


Figure 19: VALUES FROM SA

Design for load (NMOS):

We use NMOS load because it provides high gain, better headroom, easier biasing for the NMOS 2nd stage, and systematic offset cancellation

Assume $V_{INM_{MIN}} = V_{GS} - V_{THP} = 0.03V$ $\longrightarrow V_{GSn}=810m$

And assume $r_{on}=r_{op}=2M\Omega$

From SA I found:

$L = 500n$ $W=1.69u$

$gm/id=11.58$ $g_{mn} = 56.91u$

3	L	500n
4	W	1.69u
5	VGS	810m
6	VDS	600m
7	VSB	0
8	gm/ID	11.58
9	Vstar	172.7m
10	fT	3.321G
11	gm/gds	117.5

Lab 09 (Mini Project 01) Two-Stage Miller OTA



Design for the tail current source (PMOS):

PMOS inputs require a PMOS tail source at the top.

$$CMRR(db) = A_{VD}(db) - A_{vcm}(db) \quad A_{vcm} = -39db = 0.01122$$

$$A_{vcm} = \frac{1}{g_m \times R_{ss}} \rightarrow R_{ss} = 783K$$

$$V^* = V_{DD} - V_{GS} - V_{INM_MAX} \quad V^* = 130m \text{ (for some margin)}$$

$$L = 400n \quad W = 22.17u$$

$$gm/id = 15.1 \quad gm = 151 \mu$$

	Name	TT-27.0
1	ID	10u
2	IG	N/A
3	L	400n
4	W	22.17u
5	VGS	834.6m
6	VDS	600m
7	VSb	0
8	gm/ID	15.1
9	Vstar	132.5m

Figure 20: VALUES FROM SA

Design for the 2ND input pair (NMOS):

we want VGS of 1st stage load = VGS of 2nd stage input = 810 mV to eliminate systematic input-referred offset voltage

$$i_{dM6} = 40u, A_{OL(2nd \text{ stage})} = 32$$

$$SO, L = 360n \quad W = 7.1u$$

$$gm/id = 9.862 \quad gm = 400.6u$$

In a 2-stage Miller OTA, the compensation capacitor CC creates a right-half plane (RHP) zero if connected directly. By putting a resistor RZ in series with CC, you can move that zero,

$$So RZ = \frac{1}{gm \text{ (input transistor of this second stage)}} = 2.496k$$

	Name	TT-27.0
3	L	360n
4	W	7.1u
5	VGS	810m
6	VDS	900m
7	VSb	0
8	gm/ID	9.862
9	Vstar	202.8m
10	fT	6.712G
11	gm/gds	59.94

Figure 21: VALUES FROM SA

Important Note :

I made some changes to some sizes to adjust some specs, the most important of which are :

- **W_{second input pair} increased to →** boosted gm, improved phase margin.
- **W_{second input pair} increased to 3.2959u as shown →** set VDSV of 2nd-stage NMOS ≈ 0.9 V for proper bias.
- **L_{tail} increased to 420n →** reduced gds, raised output resistance, improved CMRR

 


Figure 22: VOUT VS W_LOAD

Lab 09 (Mini Project 01) Two-Stage Miller OTA



part3: open loop OTA simulation

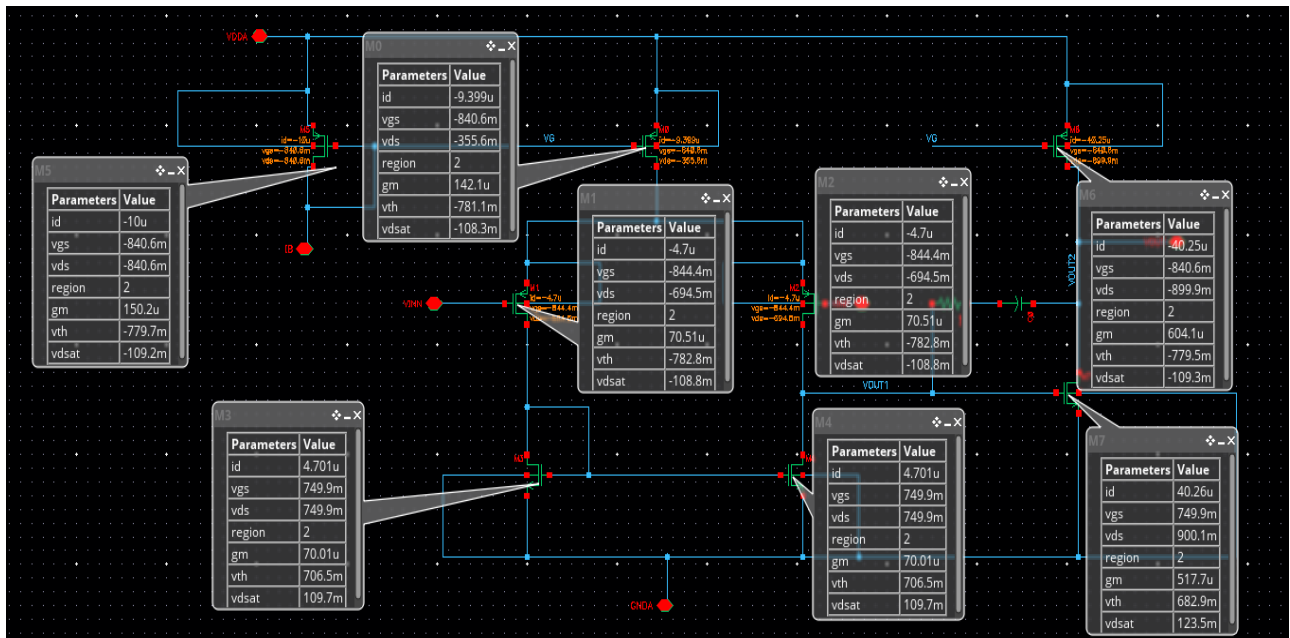


Figure 24:schematic with balloons annotated

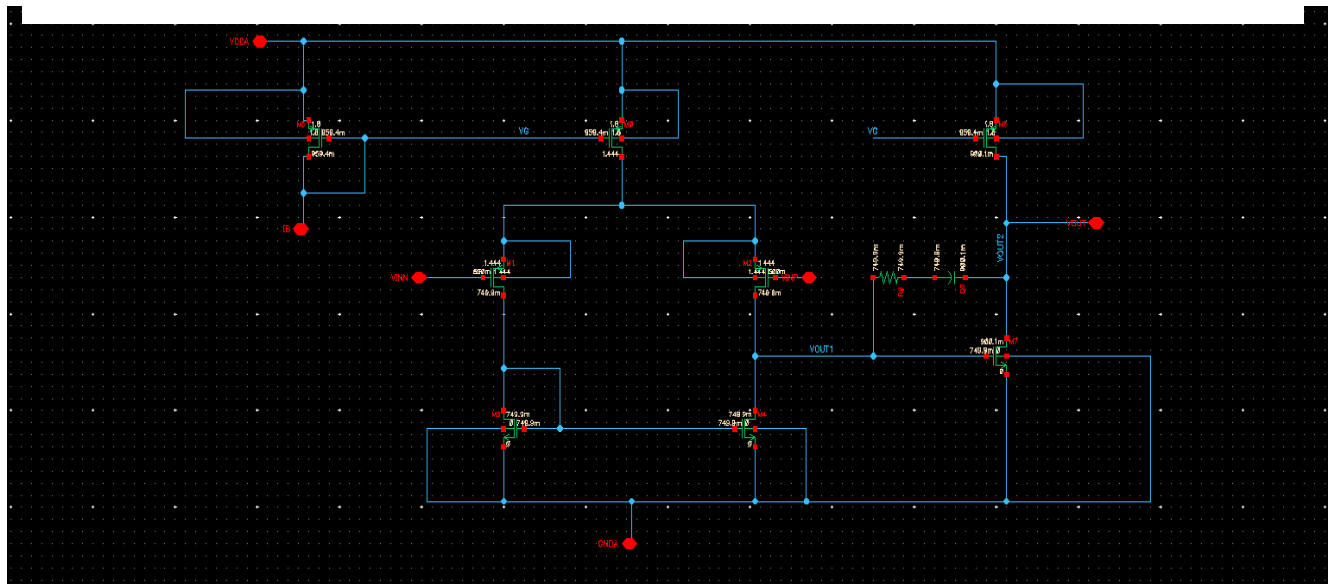


Figure 23:schematic with dc node voltages annotated

Is the current (and gm) in the input pair exactly equal?

- Yes — the currents (and therefore **gm**) in the input pair are exactly equal, since there's no mismatch. The two transistors in the input pair have the same VGS, VDS, and identical W/L

What is DC voltage at the output of the first stage? Why?

- Vout1= 749.9m, there's no mismatch, Vout1= vgs_tail=749.9m

What is DC voltage at the output of the second stage? Why?

- VOUT2= 0.9V, there's no mismatch VOUT2=VDD-VDSP=0.9V

Lab 09 (Mini Project 01) Two-Stage Miller OTA



2)Diff small signal ccs:

 


Figure 25:DIFF GAIN VS FREQ (in dB)

Test	Output	Nominal	Spec	Weight	Pass/Fail
lab_9_mini_project:part_2:1	AO	2.96k			
lab_9_mini_project:part_2:1	AO_dB	69.43			
lab_9_mini_project:part_2:1	BW	1.823k			
lab_9_mini_project:part_2:1	Fu	5.173M			
lab_9_mini_project:part_2:1	GBW	5.41M			

Figure 26: RESULTS FROM SIMULATION

Hand analysis:

$$|A_{v_{diff}}| = g_{m1} \times (r_{o1} // r_{o3}) \times g_{m7} \times (r_{o6} // r_{o7}) = 2965.41 = 69.441 \text{ dB}$$

$$BW = \frac{1}{2\pi \times C_c \times (r_{o1} // r_{o3}) \times (1 + g_{m7} \times (r_{o6} // r_{o7}))} = 1848.8 \text{ HZ}$$

$$GBW = \frac{g_{m1,2}}{2\pi \times C_c} = 5.611 \text{ MHZ} > 5 \text{ MHZ almost equal UGF}$$

	GAIN	BW	UGF	GBW
From simulation	69.43 dB	1823 HZ	5.173M	5.41M
From hand analysis	69.441 dB	1848.8 HZ	5.611M	5.611M



3)CM small signal ccs:

 


Figure 27: CM GAIN VS FREQ (In dB)

Test	Output	Nominal	Spec	Weight	Pass/Fail
lab_9_mini_project:part_2:1	AO	457.6m			
lab_9_mini_project:part_2:1	AO_dB	-6.789			

Hand analysis:


$|A_{V_{cm}}| = \frac{1}{2 \times g_{mn} \times r_{o\ tail}} g_{m_7} \times (r_{o6} // r_{o7}) = 0.4649 = -6.6522\text{ dB}$

	Simulation	Hand analysis
$ A_{V_{cm}} $	-6.789 dB	-6.6522 dB

Lab 09 (Mini Project 01) Two-Stage Miller OTA



4)CMRR:

 

From simulation:

$$\text{CMRR} = 76.216 \text{ dB} > 74 \text{ dB}$$

Hand analysis:

$$\text{CMRR (db)} = \text{AVD(db)} - \text{AVCM(db)} = 76.0932 \text{ db}$$

	Simulation	Hand analysis
CMRR	76.216 dB	76.0932 dB

Lab 09 (Mini Project 01) Two-Stage Miller OTA



5) (Optional) Diff large signal ccs:

 


Figure 28:vout vs vid

VOUT(From simulation) = 900.12 mV

VOUT(From DC OP) = 900.1 mV

This is expected because when the differential input is zero, both input transistors carry equal current, so the circuit settles to its DC bias point

 


Figure 29:deriv(vout vs vid)

Peak = 2.95958 KV which almost = Avd

Comment: The peak gain from the transient test is almost the same as the gain from the AC analysis because both are measuring the small-signal behavior of the circuit around its bias point. They are not identical since the transient method depends on the input signal amplitude and FFT calculation, which can cause small differences compared to the direct AC analysis.

Lab 09 (Mini Project 01) Two-Stage Miller OTA



6) CM large signal ccs (region vs VICM):

 


Figure 30: REGIONS VS VICM

From graph : $20\text{m} < \text{VICM} < 850\text{m}$ Which achieves our specs in the first

Hand analysis

$$\text{VICMmax} = -V_{\text{dsat0}} - v_{\text{gs1}} + v_{\text{dd}} = 847.3 \text{ mV}$$


$$\text{VICMmin} = v_{\text{gs3}} - v_{\text{gs1}} + v_{\text{dsat1}} = 15.2 \text{ mV}$$

	Hand	simulation
VICMmin	15.2 mV	20 mV
VICMmax	847.3 mV	850 mV


Lab 09 (Mini Project 01) Two-Stage Miller OTA



 7)(Optional) CM large signal ccs (GBW vs VICM):



 From graph :20m < VICM < 850m Which achieves our specs in the first



From graph :28.903m < VICM < 869.259m Which achieves our specs in the first



PART 4: Closed-Loop OTA Simulation

1) Schematic of the OTA and the bias circuit with DC OP point clearly annotated in unity gain buffer configuration.

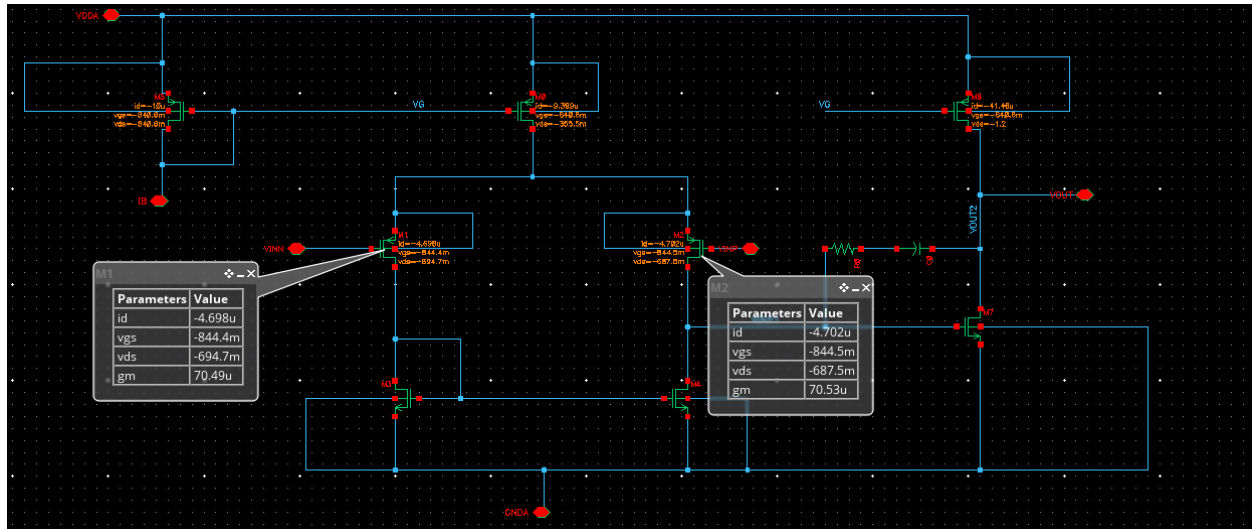


Figure 34: schematic with dc op annotated


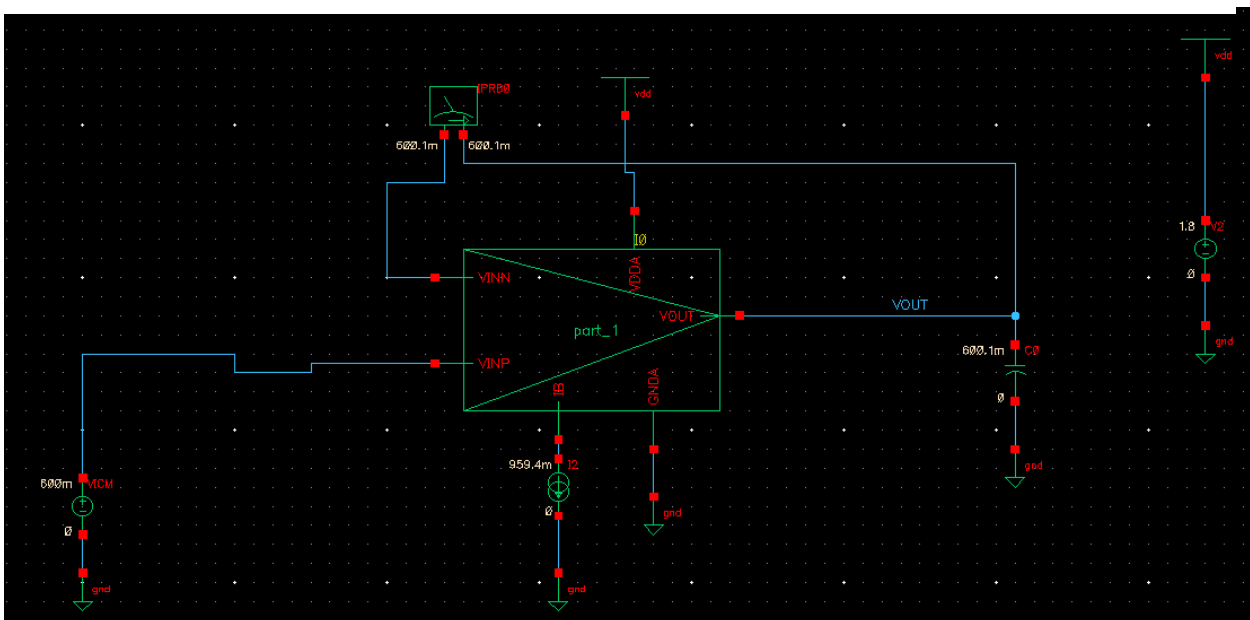


Figure 33: symbol voltages

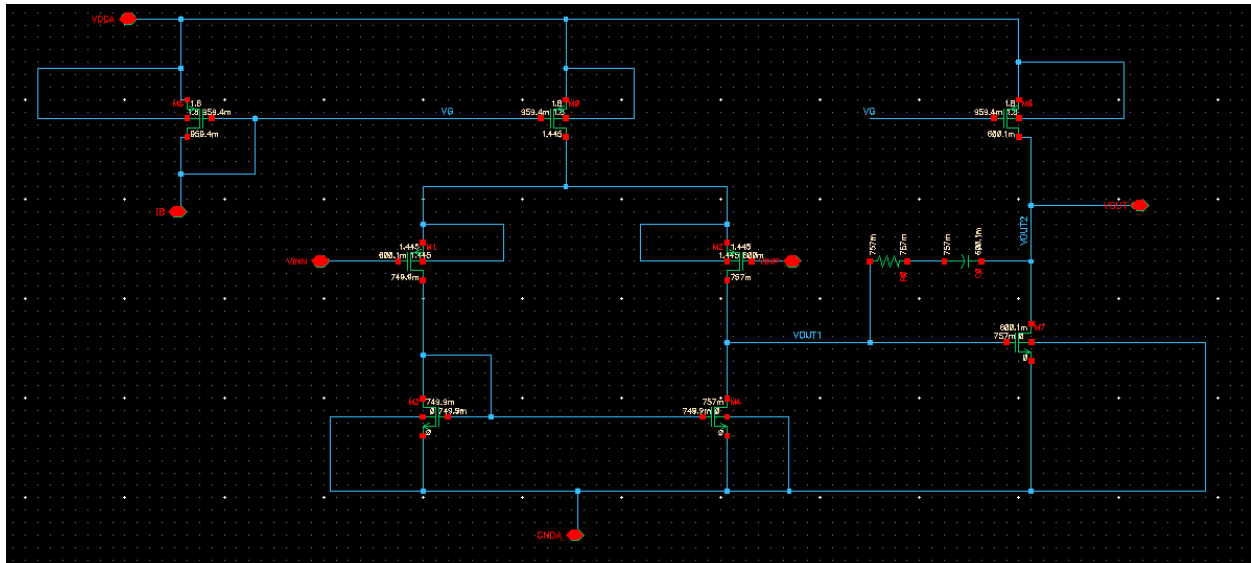

Are the DC voltages at the input terminals of the op-amp exactly equal? Why?

- Approximately Yes — in closed loop the DC voltages at the op-amp inputs are (almost) equal. This is because negative feedback forces the op-amp to adjust its output until the differential input voltage is nearly zero. With high open-loop gain, even a tiny difference between the inputs produces a large output change, so at steady state the inputs sit at the same DC potential.

Is the DC voltage at the output of the first stage exactly equal to the value in the open-loop simulation? Why?

- No, Closed loop introduces a small input error and shifts the common-mode, so the first-stage DC node moves from its open-loop value."

Is the current (and gm) in the input pair exactly equal? Why?

- No — in closed-loop operation, a small differential input voltage is required due to the OTA's finite gain, which creates an effective mismatch between the two input transistors. This mismatch causes their drain currents — and therefore their g_m — to be slightly different.

Lab 09 (Mini Project 01) Two-Stage Miller OTA



2) Loop gain:

 


Figure 37: LOOP GAIN VS FREQ

Parameters: C=2p					
1	lab_9_mini_project:part_2:1	A01	2.845k		
1	lab_9_mini_project:part_2:1	A01_dB	69.08		
1	lab_9_mini_project:part_2:1	GBW1	5.401M		
1	lab_9_mini_project:part_2:1	Fu1	5.176M		
1	lab_9_mini_project:part_2:1	phase margin DEG	73.4		

Figure 36: Result from simulation (contains PM)

Compare DC gain, fu, and GBW with those obtained from open-loop simulation. Comment

	GAIN	UGF	GBW
Open loop	69.43 dB	5.173M	5.41M
Loop gain	69.08 dB	5.176M	5.401M

DC gain is nearly the same in both cases with only a slight drop in Loop gain, while UGF and GBW are almost identical. This shows feedback has little effect on the frequency response, and differences come only from small bias/loading changes and there is mismatch when I closed the loop

Lab 09 (Mini Project 01) Two-Stage Miller OTA



Hand analysis:

$$|A_{vdiff}| = g_{m1} \times (r_{o1} // r_{o3}) \times g_{m7} \times (r_{o6} // r_{o7}) = 2847.41 = 69.089 \text{ dB}$$


$$BW = \frac{1}{2\pi \times C_c \times (r_{o1} // r_{o3}) \times (1 + g_{m7} \times (r_{o6} // r_{o7}))} = 1896.88 \text{ Hz}$$

$$GBW = \frac{g_{m1,2}}{2\pi \times C_c} = 5.4 \text{ MHz} > 5 \text{ MHz almost equal UGF}$$

$$w_2 = \frac{gm(\text{input second stage})}{2\pi \times C_l}$$

$$PM = 90 - \tan^{-1}\left(\frac{w_u}{w_2}\right) = 72.686 \text{ deg}$$

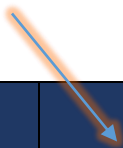The formula $PM = 90 - \tan^{-1}\left(\frac{w_u}{w_2}\right)$ assumes only two poles and no zeros. In the real OTA, extra poles/zeros, finite gain, and bias shifts are present, so the phase at unity-gain differs. That's why the simulated PM is not exactly the same as the formula result



	GAIN	PM	UGF	GBW
From simulation	69.08 dB	73.4 DEG	5.176M	5.401M
From hand analysis	69.089 dB	72.686 DEG	5.4M	5.4M

Lab 09 (Mini Project 01) Two-Stage Miller OTA



3) Slew rate:

 


Figure 38: VOUT VS VIN

Report the slew rate

Parameters: C=2p			
1	lab_9_mini_project:part_2:1	phase margin DEG	73.62
1	lab_9_mini_project:part_2:1	slew rate	4.294M

As shown slew rate didn't achieve our specs at $CC=2p$, so I will sweep on CC to see when achieve our specs and PM is correct also :

Parameters: C=1.6p			
1	lab_9_mini_project:part_2:1	phase margin DEG	69.93
1	lab_9_mini_project:part_2:1	slew rate	5.13M
Parameters: C=1.65p			
2	lab_9_mini_project:part_2:1	phase margin DEG	70.46
2	lab_9_mini_project:part_2:1	slew rate	5.013M
Parameters: C=1.7p			
3	lab_9_mini_project:part_2:1	phase margin DEG	70.98
3	lab_9_mini_project:part_2:1	slew rate	4.899M
Parameters: C=1.75p			
4	lab_9_mini_project:part_2:1	phase margin DEG	71.47
4	lab_9_mini_project:part_2:1	slew rate	4.79M
Parameters: C=1.8p			
5	lab_9_mini_project:part_2:1	phase margin DEG	71.93
5	lab_9_mini_project:part_2:1	slew rate	4.684M
Parameters: C=1.85p			
6	lab_9_mini_project:part_2:1	phase margin DEG	72.38
6	lab_9_mini_project:part_2:1	slew rate	4.581M
Parameters: C=1.9p			
7	lab_9_mini_project:part_2:1	phase margin DEG	72.81
7	lab_9_mini_project:part_2:1	slew rate	4.482M
Parameters: C=1.95p			
8	lab_9_mini_project:part_2:1	phase margin DEG	73.22
8	lab_9_mini_project:part_2:1	slew rate	4.387M

As shown PM & SR will achieve our spec at $CC=1.65p$



Hand analysis


$$\text{Slew_rate} = \frac{I_B}{CC} = 5.7 \text{ M}$$

	Simulation	Hand analysis
Slew_rate	5.013 M	5.7 M

4) Settling time:

Calculate the output rise time from simulation.

	C	riseTim...time")
1	1.650E-12	39.01E-9

 

Do you see any ringing? Why?

just a tiny overshoot with no sustained ringing because the **closed-loop step response reflects limited phase margin**. The second pole and parasitic poles/zeros add lag, so the feedback loop overshoots and rings before settling and the phase margin $< 76^\circ$

Compare simulation results with hand calculations in a table

HAND ANALYSIS: $T_{\text{rise}} = \frac{2.2}{2\pi \times GBW} = 64.84 \text{ ns}$

The simulation result will be better than expected. Why? Using $\text{trise} = 2.2\tau$ is based on first-order model but our second order system is faster and that clarify the difference between simulation and hand analysis

	Simulation	Hand analysis
T_{rise}	39.01 ns	64.84 ns

Lab 09 (Mini Project 01) Two-Stage Miller OTA



	Specs	Achieved specs	
Static gain error	$\leq 0.05\%$	0.03%	✓
CMRR @ DC	$\geq 74\text{dB}$	76.216dB	✓
Phase margin (avoid pole-zero doublets)	$\geq 70^\circ$	73.62°	✓
OTA current consumption	$\leq 60\mu\text{A}$	49.65 μA	✓
CMIR – high	$\geq 0.8\text{V}$	0.85 V	✓
CMIR – low	$\leq 0.2\text{V}$	0.02 V	✓
Buffer closed loop rise time (10% to 90%)	$\leq 70\text{ns}$	64.84 ns	✓
Slew_rate	$5\text{V}/\mu\text{s}$	$5\text{V}/\mu\text{s}$	✓



Part 5 (optional): DC Closed Loop AC Open-Loop OTA Simulation

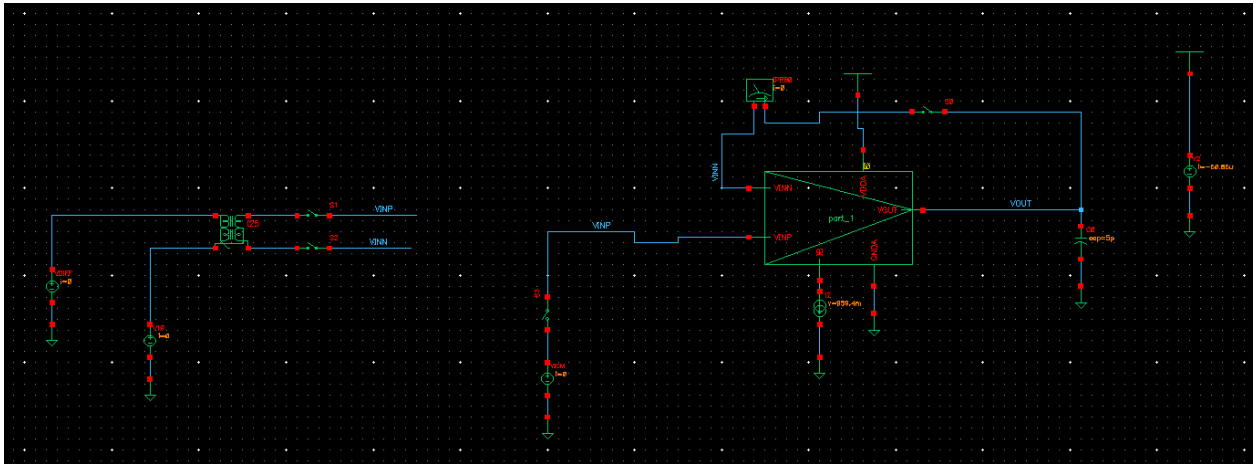


Figure 39:schematic

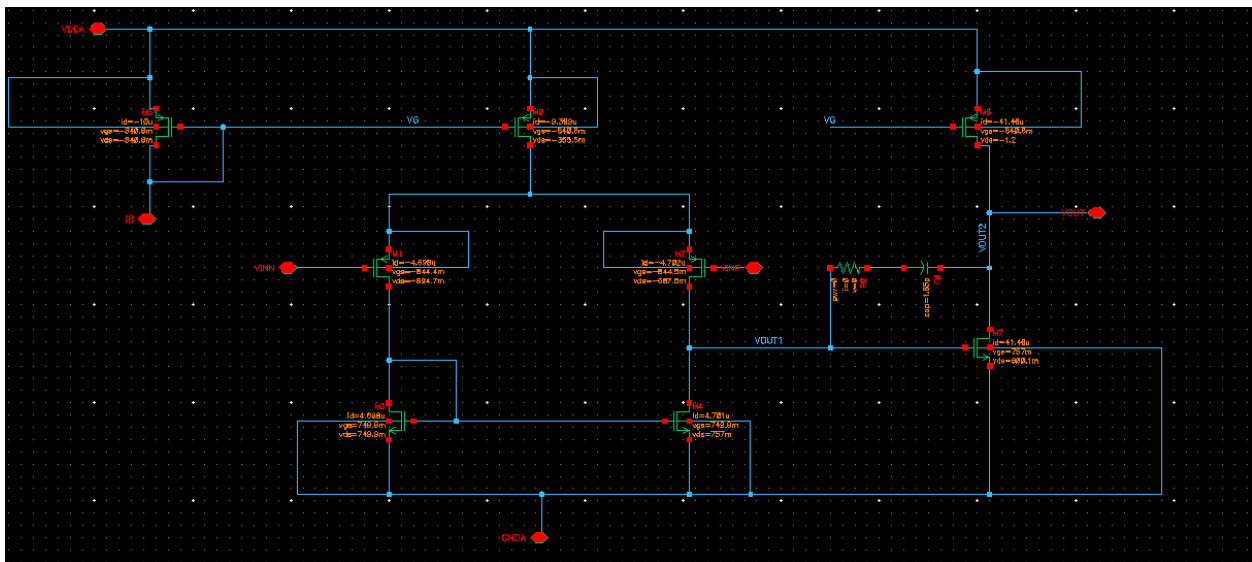


Figure 40: dc op annotated

Lab 09 (Mini Project 01) Two-Stage Miller OTA



Sat Aug 23 07:11:14 2025 1

 


Figure 43: AVDIFF vs FREQ

 


Figure 42: AVcm VS freq

 


Figure 41: CMRR

Acm dropped because closing the loop for the DC operating point changed the amplifier's bias and loop action so the circuit responds less to common-mode inputs and mismatch



Part 6 (optional): RZ Implementation

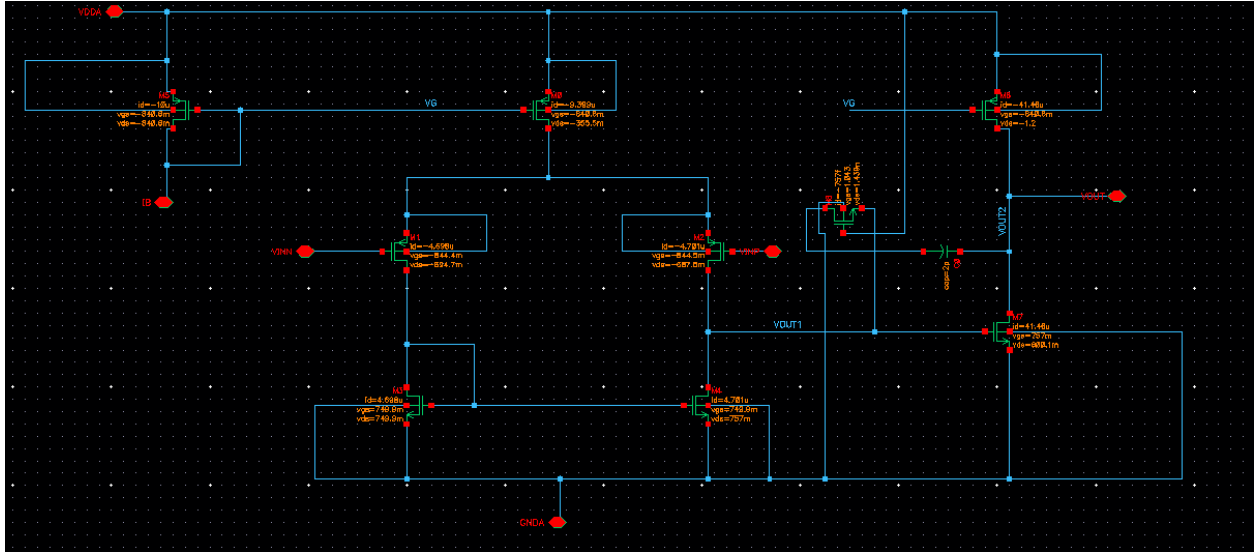


Figure 44: schematic with dc op

DC Analysis 'dc': WZ = (1e-06 -> 10e-06)

 


Figure 45: ROUT VS W

Lab 09 (Mini Project 01) Two-Stage Miller OTA



1

 


Figure 46: LOOP GAIN VS FREQ

Test	Output	Nominal	Spec	Weight	Pass/Fail
lab_9_mini_project:part_2:1	A01	2.845k			
lab_9_mini_project:part_2:1	A01_dB	69.08			
lab_9_mini_project:part_2:1	GBW1	5.398M			
lab_9_mini_project:part_2:1	Fu1	5.161M			
lab_9_mini_project:part_2:1	phase margin DEG	73.43			

NOTE I calc these values at $CC=2p$, as before changing it