

## Part 1: gm/ID Design Charts

1) For  $L = 0.28\mu$

**PMOS:**

 


Figure 1: intrinsic gain

 


Figure 2: ID/W

 


Figure 5:GM/CGG

 


Figure 4:VGS

## NMOS

 


Figure 3: intrinsic gain

 


Figure 8:  $ID/W$

 


Figure 7:  $GM/CGG$

 


Figure 6:  $V_{GS}$

For  $L=0.4\mu:0.4\mu:2\mu$

**PMOS:**

 


Figure 9:intrinsic gain

 


Figure 10:ID/W

 


Figure 12:GM/CGG

 


Figure 11:VGS

## NMOS:

 


Figure 13: intrinsic gain

 


Figure 16: $i_d/w$

 


Figure 15: $GM/C_{GG}$

 


Figure 14: $V_{GS}$

## Part 2: OTA Design

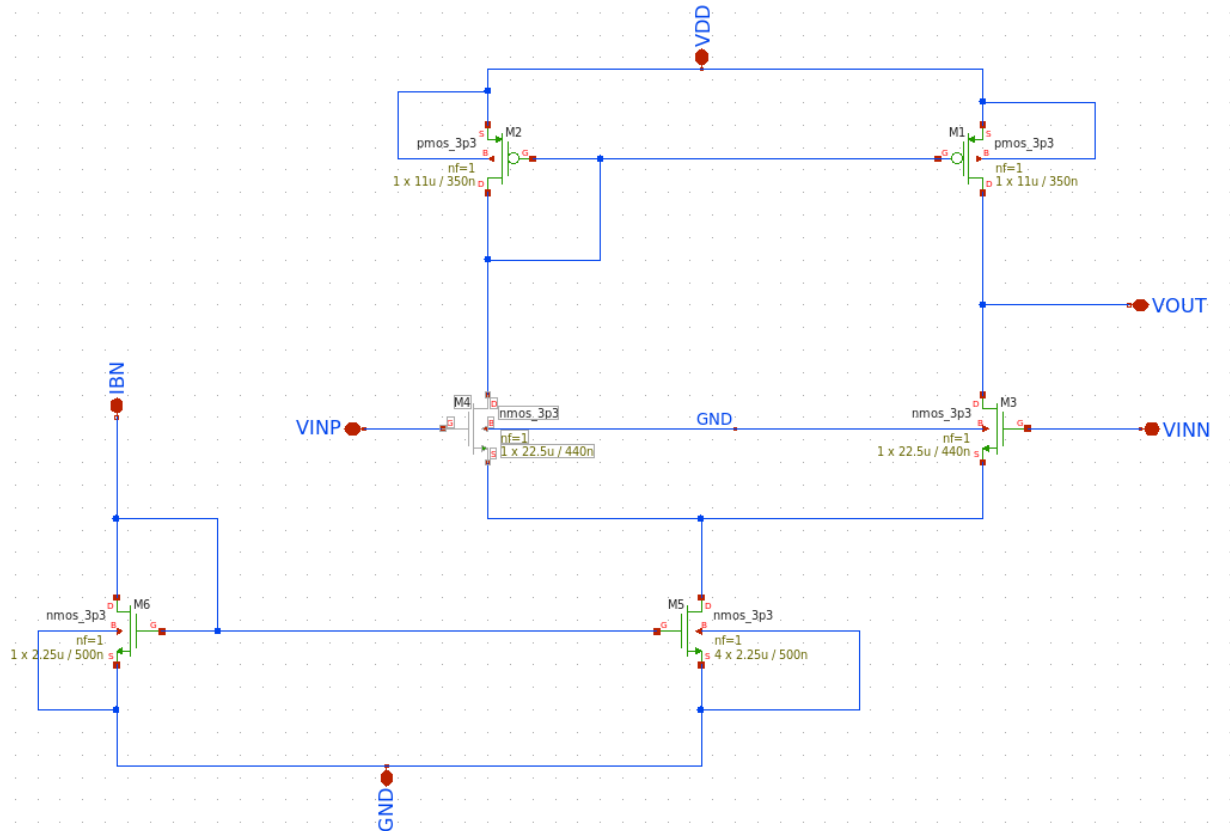


Figure 17:SCHEMATIC

- To maximize input common-mode range near VDD, an NMOS input pair was selected because NMOS transistors naturally allow operation closer to the positive supply rail than PMOS transistors

## Design for input pair (NMOS):


$$|A_V| = g_{m_n} \times (r_{on} // r_{op}) \text{ assume } r_{on} = r_{op} \rightarrow |A_V| = 0.5 \times g_{m_n} \times r_{on} \geq 50$$

$$GBW = \frac{g_m}{2\pi \times C_L} \geq 10M \rightarrow g_m \geq 2\pi \times C_L \times 10M = 0.000314$$

$$\text{Assume current } i_d = 20\mu \rightarrow \frac{g_m}{i_d} \geq 5\pi \geq 15.7$$

And for some margin I will take  $\frac{g_m}{i_d} = 17$

 Assuming  $v_{ds}$  on M4 and M2 = 0.7 and on M5(tail) = 0.4 to reduce body effect



I will choose  $L = 440n$  [M4, M3]

And from ADT I will get W

Name	TT-27.0		
4 W	22.51u	16 gm	337u
5 VGS	828.3m	17 gmb	90.81u
6 VDS	700m	18 gds	3.232u
7 VSB	400m	19 ro	309.4k
8 gm/ID	16.85	20 Ron	35k
9 Vstar	118.7m	21 VTH	819.8m
10 ft	1.94G	22 VDSAT	92.63m
11 gm/gds	104.3	23 cgg	27.65f
12 VA	6.187	24 cdd	15.76f

AS shown:  $W = 22.5\mu$  [M4, M3]

$V_{thn} = 0.8198V$



## Design for load (PMOS):

$$V_{ICMmax} < V_{DD} - V_{SG} + V_{THn}$$

$$V_{SG} \leq 1.1198$$


$$\text{Assume } r_{op} = r_{on}$$

$$0.5 \times g_{m_n} \times r_{op} \geq 50$$

$$r_{op} = \frac{V_A}{I_D} \geq \frac{50 \times 2}{g_{m_n}}$$


$$V_A \geq 5.93$$

And assume  $g_{m/id}=10$

 

As shown to satisfy
 
$$V_A \geq 5.93 \quad \text{I will take } L = 350n$$



Chosen L satisfy  $V_{SG} \leq 1.1198$

After putting values we got in SA we will find

Name	TT-27.0	Name	TT-27.0
4 W	10.88u	13 ID/W	1.838
5 VGS	920.5m	14 gm/W	18.22
6 VDS	700m	15 AREA	3.808p
7 VSB	0	16 gm	198.2u
8 gm/ID	9.912	17 gmb	77.1u
9 Vstar	201.8m	18 gds	2.728u
10 fT	2.013G	19 ro	366.6k
11 gm/gds	72.67	20 Ron	35k
12 VA	7.331	21 VTH	765.4m


I choose **W=11u**

### Design for the tail current source (NMOS):

$$\text{VICMmin} \leq \text{VGSn} + \text{VDSat} \quad \longrightarrow \quad \text{VDSat} \leq \text{VICMmin} - \text{VGSn}$$

$$\text{VDSat} \leq 1 - 0.8283 \quad \longrightarrow \quad \text{VDSat} \leq 0.1717$$

Assume  $\text{gm/id} = 10$

 

I will choose **L = 500n**

From SA :

Name	TT-27.0	Name	TT-27.0
13 ID/W	4.287	3 L	500n
14 gm/W	42.58	4 W	9.33u
15 AREA	4.665p	5 VGS	846.4m
16 gm	397.3u	6 VDS	700m
17 gmb	142.4u	7 VSB	0
18 gds	3.335u	8 gm/ID	9.932
19 ro	299.8k	9 Vstar	201.4m
20 Ron	17.5k	10 fT	4.048G
21 VTH	710m	11 gm/gds	119.1

I WILL Choose **W=9u**

Parameter	Input pair <b>M3,M4</b>	Load <b>M2 ,M1</b>	tail current source <b>M5</b>	tail current source <b>M6</b>
W	22.5u	11u	9u	2.25u
L	440n	350n	500n	500n
GM	340uS	200uS	400uS	400uS
ID	20uA	20uA	40uA	10uA
GM/ID	17	10	10	10
V*	117.29 mV	193.5 mV	202.93 mV	203.834 mV
VDSat	91 mV	171.9 mV	175.5 mV	175.9 mV
Vov	8.112 mV	145.9 mV	142 mV	142 mV

After that I made new schematic because problem with X schem so you will find

M1, M2 input pair

M4, M6 LOAD

M3, M5 tail current source

## Part 3: Open-Loop OTA Simulation


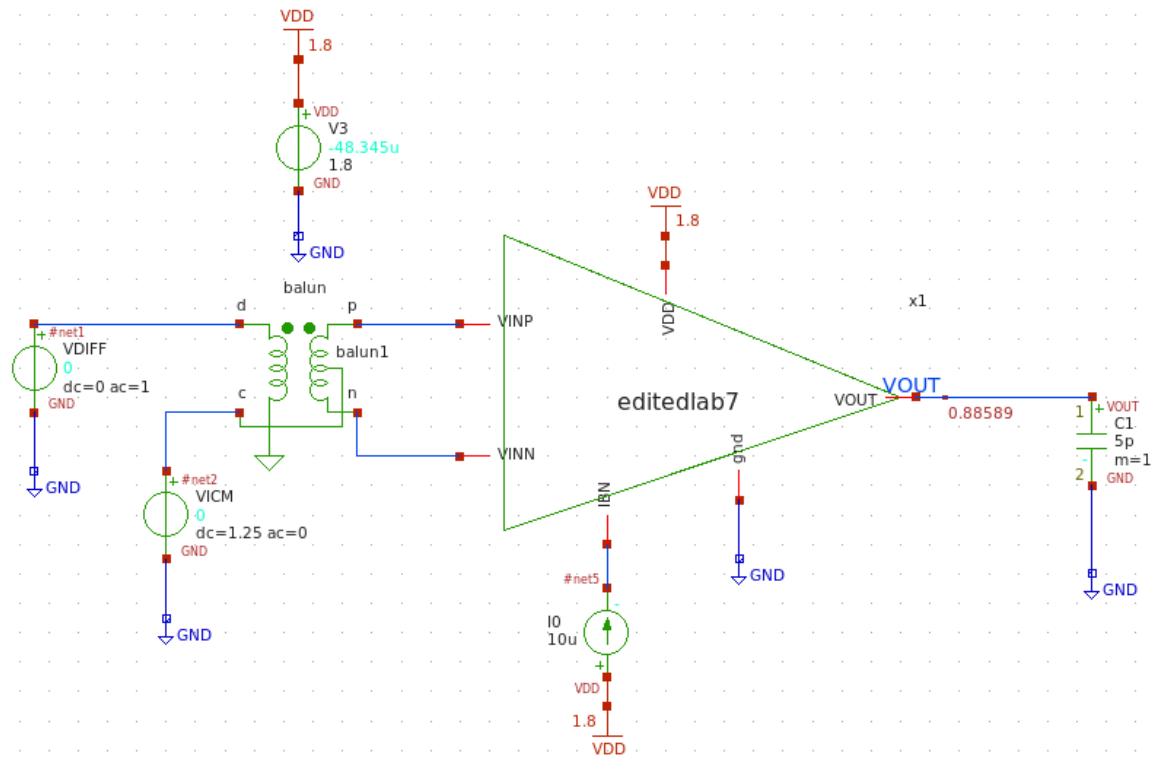


Figure 18:symbol
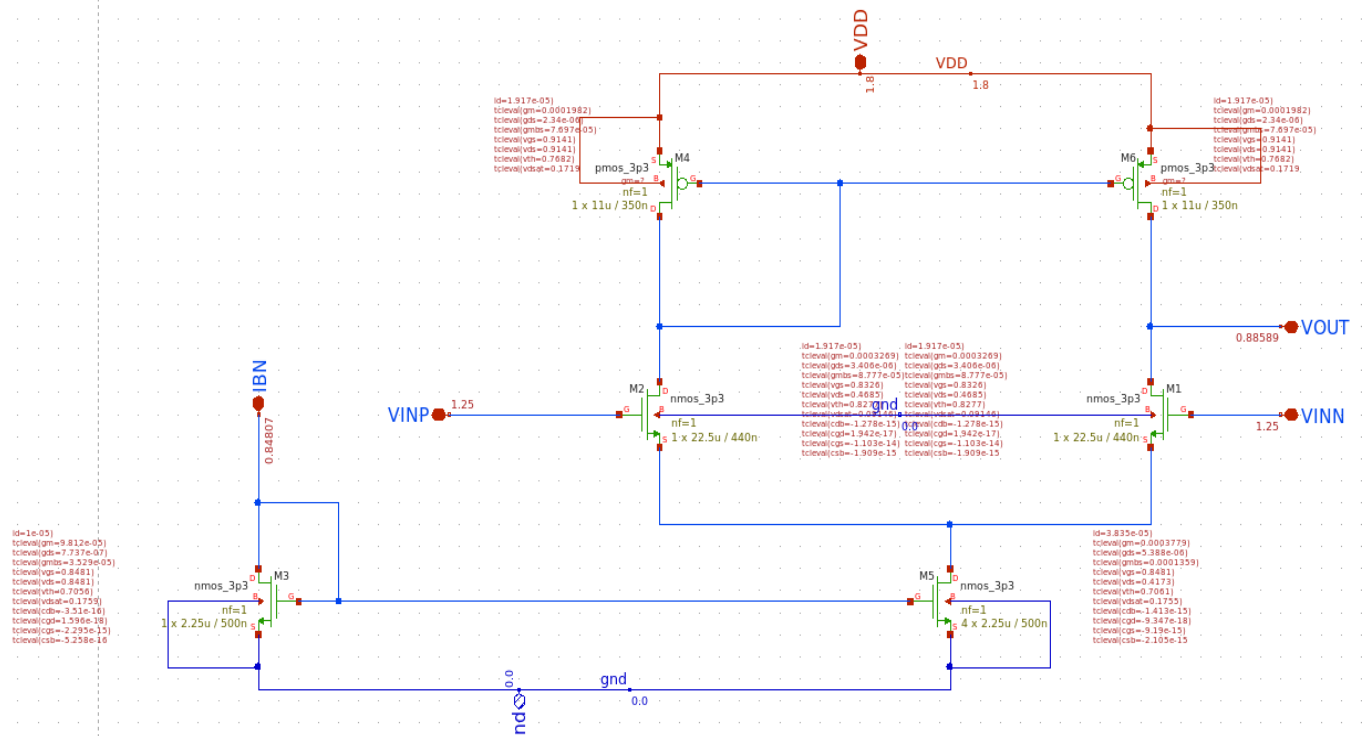
### 1) Schematic of the OTA with DC node voltages clearly annotated.



values from interactive:

BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm6.m0	m.x1.xm4.m0	m.x1.xm3.m0
model	pmos_3p3.12	pmos_3p3.12	nmos_3p3.8
id	1.91726e-05	1.91726e-05	1e-05
gm	0.000198166	0.000198166	9.81192e-05
gds	2.33988e-06	2.33988e-06	7.73674e-07
vgs	0.914109	0.914109	0.848062
vth	0.768215	0.768215	0.705603
vds	0.914107	0.914107	0.848056
vdsat	0.171919	0.171919	0.175871
BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm5.m0	m.x1.xm2.m0	m.x1.xm1.m0
model	nmos_3p3.8	nmos_3p3.12	nmos_3p3.12
id	3.83452e-05	1.91726e-05	1.91726e-05
gm	0.000377915	0.000326933	0.000326933
gds	5.38805e-06	3.40636e-06	3.40636e-06
vgs	0.848062	0.832643	0.832643
vth	0.706113	0.827703	0.827703
vds	0.417345	0.468531	0.468531
vdsat	0.175497	0.0914581	0.0914581

Is the current (and gm) in the input pair exactly equal?

Yes — the currents (and therefore **gm**) in the input pair are exactly equal, since there's no mismatch. the two transistors in the input pair have the same VGS,VDS, and identical W/L

What is DC voltage at VOUT? Why?

0.88589, there's no mismatch and  $V_{OUT} = 1.8 - v_{gs} = 1.8 - 0.914109 = 0.88589$

## 2)Diff small signal ccs:

 


Figure 19:DIFF GAIN VS FREQ (IN db)

From simulation:

```
gain      = 5.656023e+01 at= 1.000000e+00
bw        = 1.807540e+05
GBW = 1.02235E+07
```

Hand analysis:


$$|A_{vdiff}| = g_{m_n} \times (r_{on} // r_{op}) = 56.89 = 35.1 \text{ db}$$

$$BW = \frac{1}{2\pi \times C_L \times (r_{on} // r_{op})} = 182.909 \text{ KHZ}$$

$$GBW = \frac{g_m}{2\pi \times C_L} = 10.4 \text{ MHZ} > 10 \text{ MHZ}$$

	GAIN	BW	GBW
FROM SIMULATION	35.05 db	180.754 KHZ	10.22 MHZ
FROM HAND ANALYSIS	35.1 db	182.909 KHZ	10.4 MHZ

### 3)CM small signal ccs:

 


cmgain = 1.043745e-02 at= 1.000000e+00

HAND analysis:

$$|A_{V_{cm}}| = \frac{1}{2 \times g_{mp} \times r_{o \text{ tail}}} = 0.01359 = -37.33 \text{ dB}$$

	simulation	Hand analysis
$ A_{V_{cm}} $	-39.63 db	-37.33 db

### 4)CMRR:

 

Hand analysis:

$$\text{CMRR (db)} = \text{AVD(db)} - \text{AVCM(db)} = 72.43 \text{ db}$$

	simulation	Hand analysis
CMRR	74.68 db	72.43 db

### 5) Diff large signal ccs:


 


Figure 20:  $V_{OUT}$  VS  $V_{ID}$

At  $V_{ID}=0$ ,  $V_{out}=0.8859$  V because:

 The diode-connected PMOS load sets  $V_{out}=V_{DD}-V_{GS,p}$  with  $V_{DD}=1.8$  V and  $V_{GS,p}\approx 0.9141$  V, the output settles to 0.8859 V (DC bias point). Confirms no systematic offset (balanced input pair and current mirror) and  $V_{ID} = 0$ , the output simply settles to the OTA's internal bias (diode/mirror node) voltage set by the bias network and device sizing




Peak = 55.89 V which almost =  $A_{vd}$



## 6) CM large signal ccs (GBW vs VICM):

GBW VS VICM

 


Values from interaction :

```
gain          = 1.293584e+00 at= 1.000000e+00
bw            = 4.240433e+06
max_gbw       = 1.031222e+07 at= 2.511886e+07
min_vincm     = 9.044883e-01
max_vincm     = 1.692378e+00
min_vincm = 9.044883e-01
max_vincm = 1.692378e+00
cmir = 7.878897e-01
```

$0.904 < \text{VICM} < 1.69$  Which achieves our specs in the first

The schematic shows a DAC core block labeled 'editedlab7' with three inputs: V<sub>INP</sub>, V<sub>INN</sub>, and I<sub>BIAS</sub>. The output is V<sub>OUT</sub>, which is connected to a load capacitor C<sub>1</sub> (5pF) and a resistor R<sub>1</sub> (10kΩ) to ground. The I<sub>BIAS</sub> input is connected to a current source I<sub>0</sub> (10uA) and a resistor R<sub>2</sub> (10kΩ) to ground. The V<sub>INN</sub> input is connected to a voltage source V<sub>3</sub> (1.8V) and a resistor R<sub>3</sub> (10kΩ) to ground. The V<sub>INP</sub> input is connected to a voltage source V<sub>1</sub> (1.05V) and a resistor R<sub>4</sub> (10kΩ) to ground. The output V<sub>OUT</sub> is also connected to a voltage source V<sub>2</sub> (1.8V) and a resistor R<sub>5</sub> (10kΩ) to ground. The circuit is powered by VDD and GND.

[illegible]

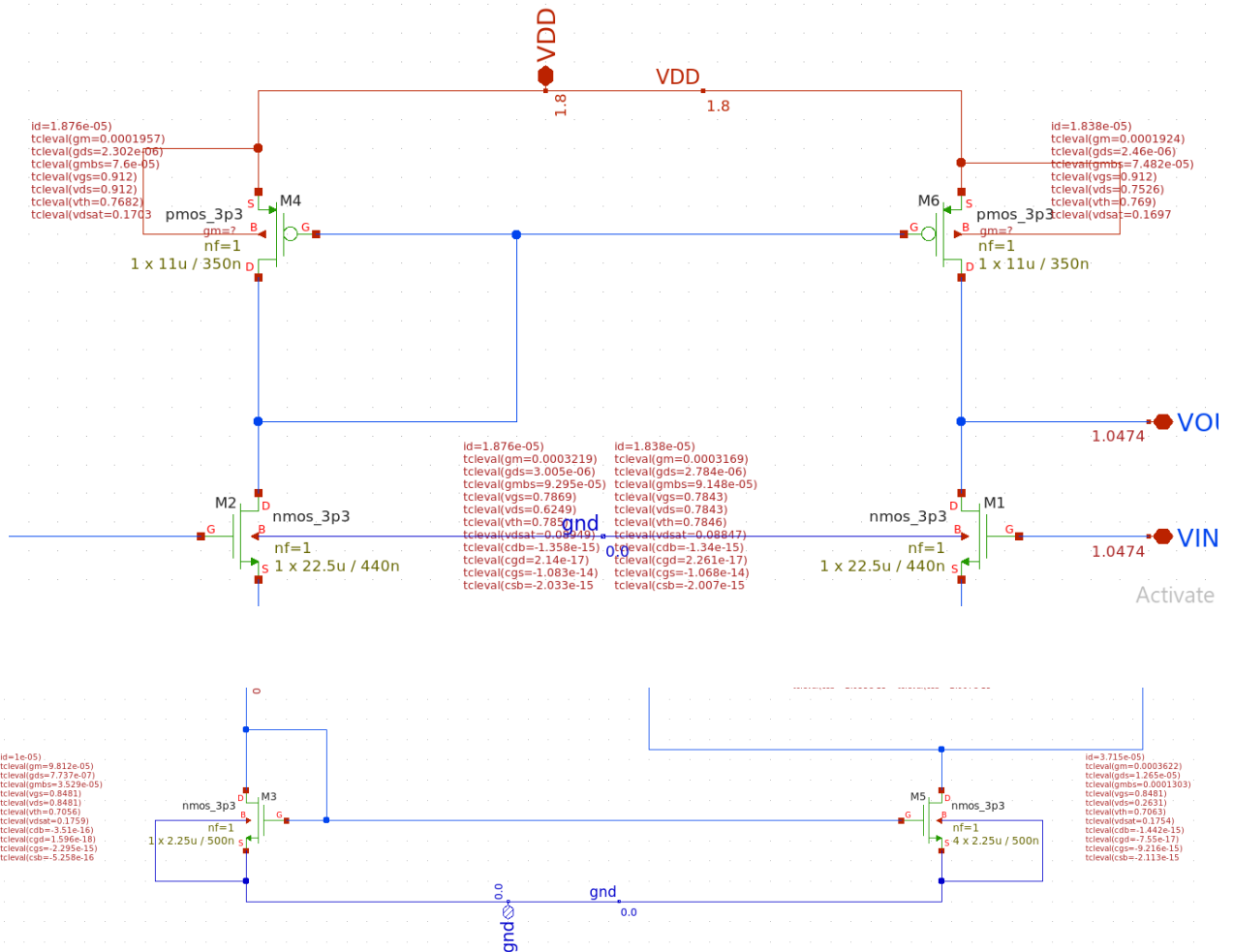

values from interactive :

device	m.x1.xm6.m0	m.x1.xm4.m0	m.x1.xm3.m0
model	pmos_3p3.12	pmos_3p3.12	nmos_3p3.8
id	1.83831e-05	1.87619e-05	1e-05
gm	0.000192435	0.000195683	9.81192e-05
gds	2.46028e-06	2.3015e-06	7.73674e-07
gmb	7.48246e-05	7.59959e-05	3.52911e-05
vgs	0.912048	0.912048	0.848062
vth	0.769037	0.768225	0.705603
vds	0.752622	0.912046	0.848056

device	m.x1.xm5.m0	m.x1.xm2.m0	m.x1.xm1.m0
model	nmos_3p3.8	nmos_3p3.12	nmos_3p3.12
id	3.71451e-05	1.87619e-05	1.83831e-05
gm	0.000362193	0.000321936	0.000316894
gds	1.2655e-05	3.00486e-06	2.78364e-06
gmb	0.000130348	9.29508e-05	9.14755e-05
vgs	0.848062	0.786906	0.78428
vth	0.706296	0.785008	0.78455
vds	0.263082	0.624855	0.784279

Is the current (and gm) in the input pair exactly equal<sup>1</sup>? Why?

No — in closed-loop operation, a small differential input voltage is required due to the OTA's finite gain, which creates an effective mismatch between the two input transistors. This mismatch causes their drain currents — and therefore their gm — to be slightly different.

Calculate the mismatch in  $I_D$  and gm.

The mismatch in input pair M1,M2 and after getting values from interactive will be :

### 1. Input Pair (M1 vs M2)

Transconductance (gm)

- $gm_{M1} = 316.894 \mu S$
- $gm_{M2} = 321.936 \mu S$
- $gm_{\text{no mismatch}} = \text{Average}(326.933, 326.933) = 326.933 \mu S$

$$\text{gm Mismatch} = \frac{316.894 - 321.936}{326.933} \times 100 = \boxed{-1.54\%}$$

Current (ID)

- $ID_{M1} = 18.3831 \mu A$
- $ID_{M2} = 18.7619 \mu A$
- $ID_{\text{no mismatch}} = \text{Average}(19.1726, 19.1726) = 19.1726 \mu A$

$$\text{ID Mismatch} = \frac{18.3831 - 18.7619}{19.1726} \times 100 = \boxed{-1.98\%}$$

### 2. Current Mirror Load (M4 vs M6)

Transconductance (gm)

- $gm_{M4} = 195.683 \mu S$
- $gm_{M6} = 192.435 \mu S$
- $gm_{\text{no mismatch}} = \text{Average}(198.166, 198.166) = 198.166 \mu S$

$$\text{gm Mismatch} = \frac{195.683 - 192.435}{198.166} \times 100 = \boxed{1.64\%}$$

Current (ID)

- $ID_{M4} = 18.7619 \mu A$
- $ID_{M6} = 18.3831 \mu A$
- $ID_{\text{no mismatch}} = \text{Average}(19.1726, 19.1726) = 19.1726 \mu A$

$$\text{ID Mismatch} = \frac{18.7619 - 18.3831}{19.1726} \times 100 = \boxed{1.98\%}$$

## 2) Loop gain

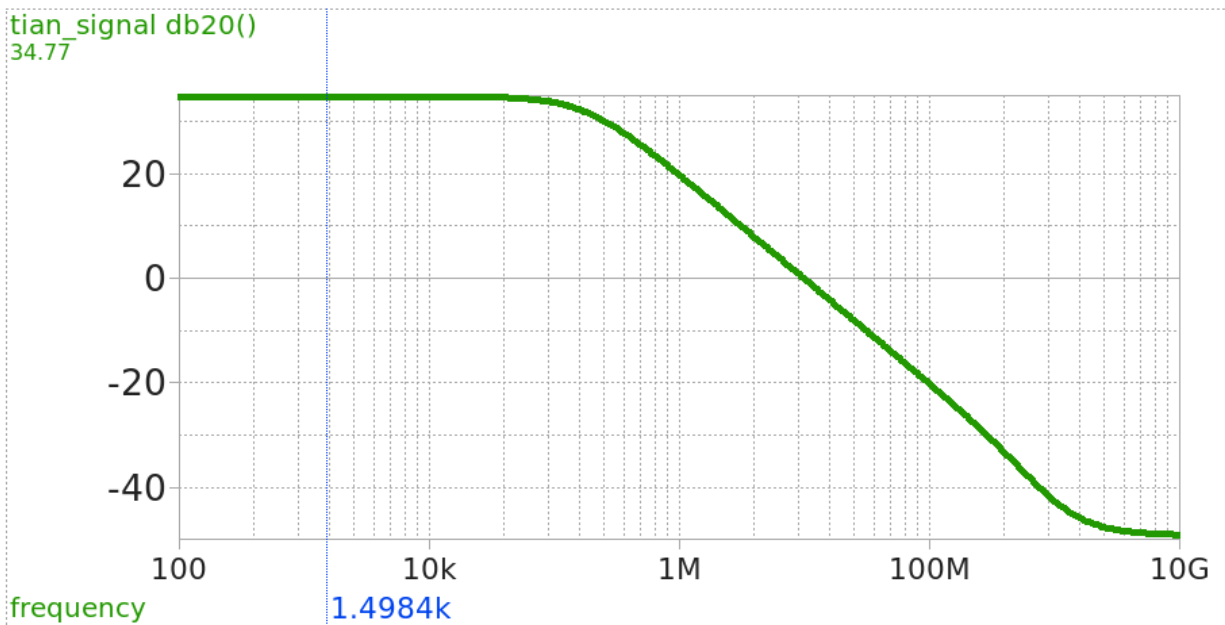
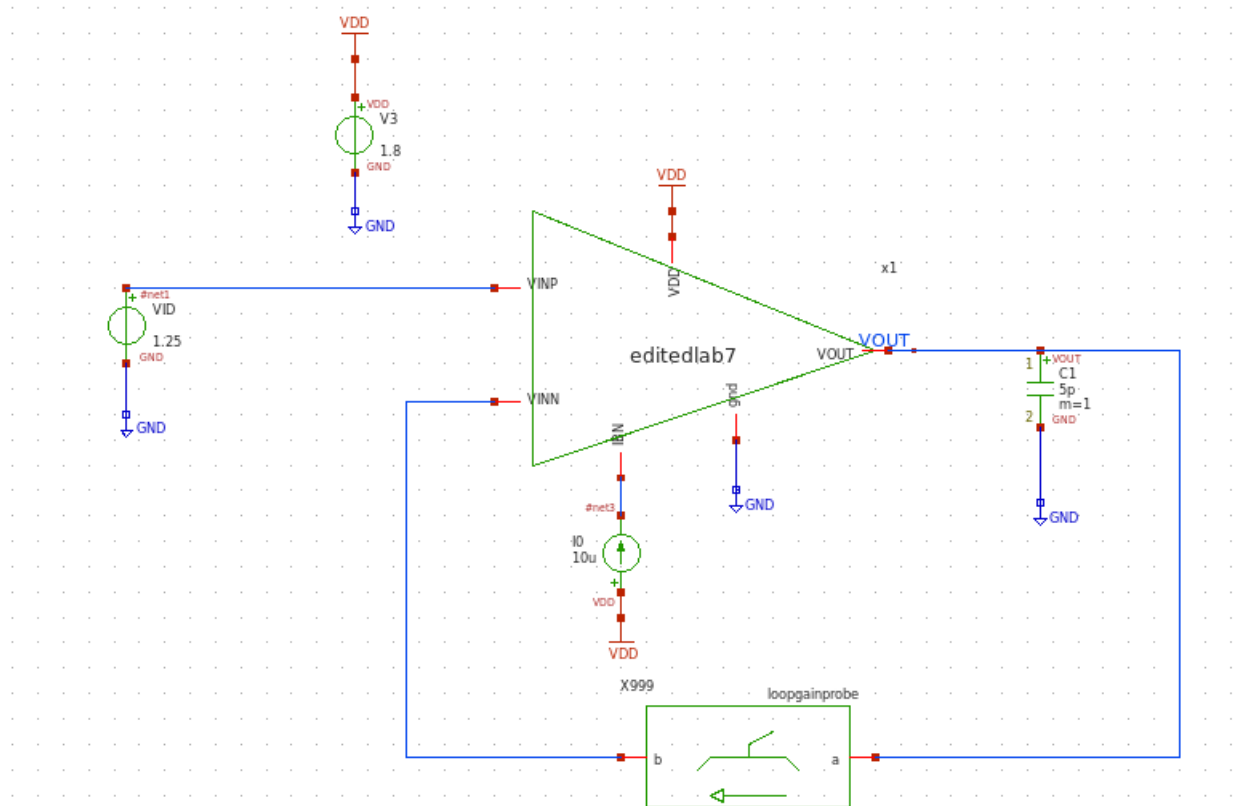


Figure 21: GAIN VS FREQ (in db)

 


Figure 22:gain (-3db) vs freq

 


Figure 23:phase vs freq

From interactive :

```
gain_crossover_freq = 9.881904e+06
phaseatzerogain      = 9.031480e+01
pm = 8.968520e+01
```

(For closed loop):

From simulation

$$|A_v| = \frac{A_{open\ loop}}{1+LG} = \frac{56.56}{1+54.76} = 1.01$$

$$BW = BW_{open\ loop} \times (1 + LG) = 194.42\ K \times (1 + 54.76) = 10.84\ MHz$$

$$GBW = 10.95\ MHz$$

Hand analysis:

$$|A_v| = \frac{A_{open\ loop}}{1+LG} = \frac{56.89}{1+56.89} = 0.98$$

$$BW = BW_{open\ loop} \times (1 + LG) = 194.42\ K \times (1 + 56.89) = 10.588\ MHz$$

$$GBW = 10.378\ MHz$$

	GAIN	BW	GBW	GAIN	BW	GBW
	CLOSED LOOP			OPEN LOOP		
FROM SIMULATION	1.01	10.84 MHz	10.95 MHz	56.56	194.42 KHZ	10.22 MHz
FROM HAND ANALYSIS	0.98	10.588 MHz	10.378 MHz	56.89	182.909 KHZ	10.4 MHz

## Comment

With  $\beta = 1$ , the loop gain is equal to the open-loop gain. According to feedback theory, closing the loop reduces the closed loop gain by a factor of  $1+LG$  while increasing the bandwidth by the same factor. This trade-off keeps the gain–bandwidth product nearly constant. **Since  $\beta = 1$ , the measured loop gain and bandwidth changes directly match the open-loop values**, confirming that the GBW remains essentially the same in both cases.

	Specs	Achieved specs	
Open loop DC voltage gain	$\geq 34\text{dB}$	35.05 dB	✓
CMRR @ DC <sup>1</sup>	$\geq 74\text{dB}$	74.68 dB	✓
Phase margin	$\geq 70^\circ$	90.31 °	✓
CM input range – low	$\leq 1\text{V}$	0.904 V	✓
CM input range – high	$\geq 1.5\text{V}$	1.69 V	✓
GBW	$\geq 10\text{MHz}$	10.22 MHz	✓