

Analog IC Design – Cadence Tools

Lab 02

Common Source Amplifier

PART 1: Sizing Chart:

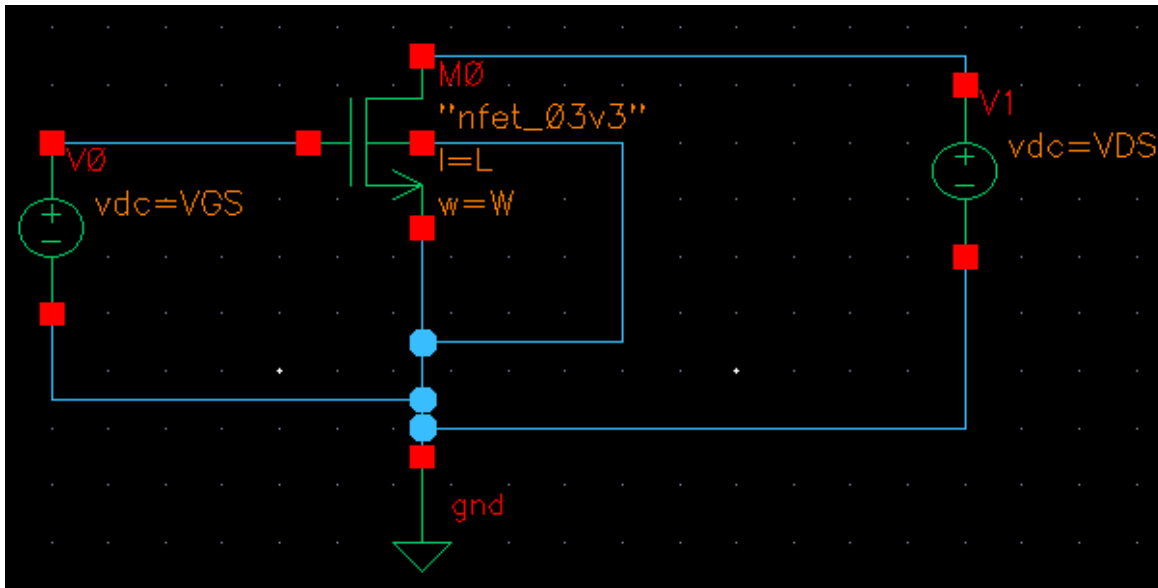


Figure 1: schematic

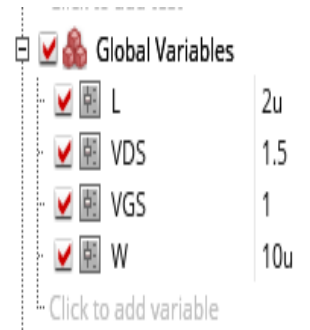


Figure 2: values of Variables

spec	0.18um CMOS
DC Gain	-12
Supply	3 V
Current consumption	200 μA

Figure 3: edited spec

Hand analysis:

$$|A_V| = \frac{g_m}{I_D} R_D I_D = \frac{g_m}{I_D} \times \frac{V_{DD}}{2} = 12 \quad \longrightarrow \quad I_D R_D = \frac{V_{DD}}{2} = 1.5 \quad \longrightarrow \quad \text{SO, } R_D = 7.5 \text{ K}\Omega$$





$$V^* = \frac{2I_D}{g_m} \quad \text{and} \quad |A_V| = \frac{V_{RD}}{V^*} \quad \longrightarrow \quad \text{SO, } V^* = 250 \text{ mV}$$

`2 * (getData("M0:id" ?result "dc") / getData("M0:gm" ?result "dc"))`

Figure 4: Expression to calc (V^*)

`v("M0:vgs" ?result "dc") - v("M0:vth" ?result "dc")`

Figure 5: Expression to calc (V_{ov})

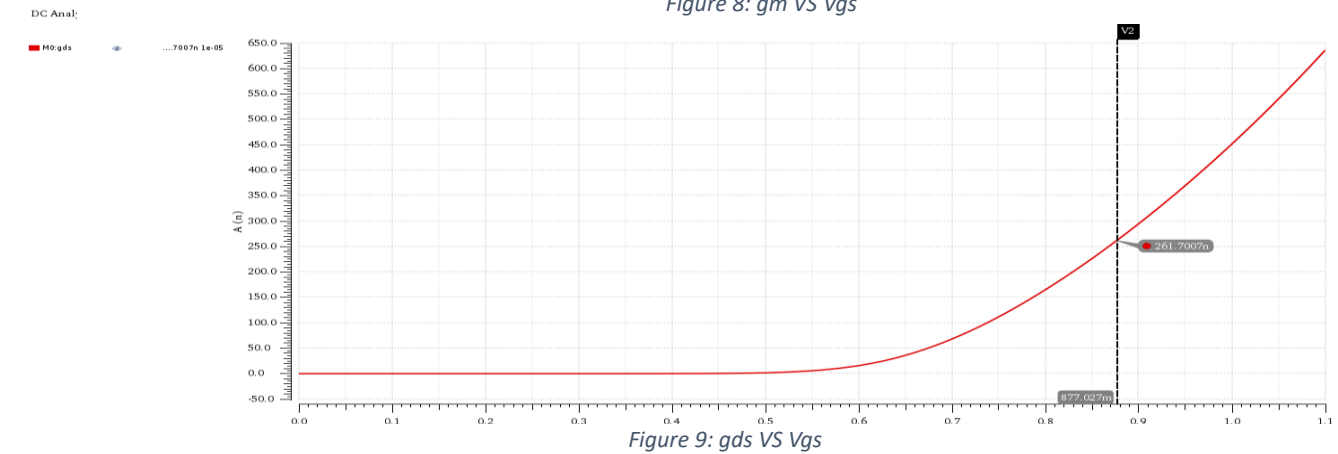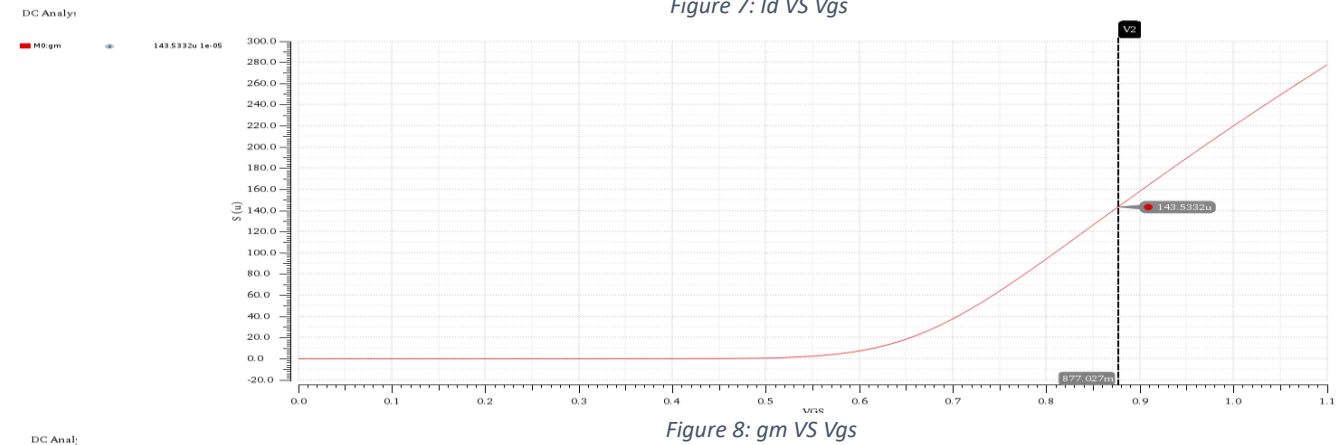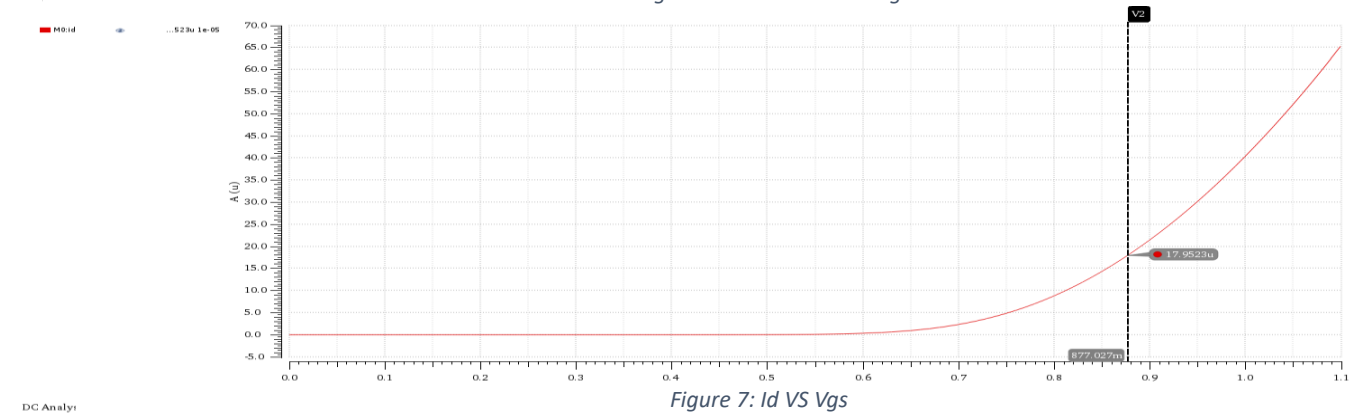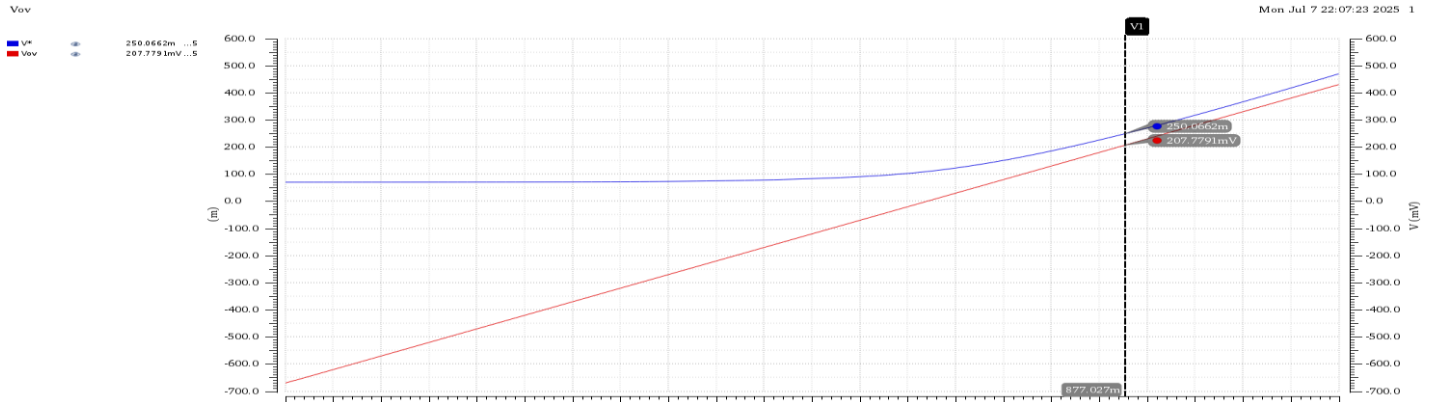

From graphs the required value will be:

1-

V^*	250 mV
R_D	7.5 K Ω
V_{ovQ}	207.7791 mV
V_{GSQ}	877.027 mV
I_{Dx}	17.9523 μA
g_{mx}	143.5332 μS
g_{dsx}	261.7007 nS
V_{th}	669 mV


2-

W	I_d
10 μm	17.9523 μA
111.406 μm	200 μA

3-

g_m	1.599 mS
g_{ds}	2.9155 μS
r_o	342.9943 K Ω
gain with r_o	-11.73588
gain without r_o	-11.9925

PART 2: CS Amplifier:

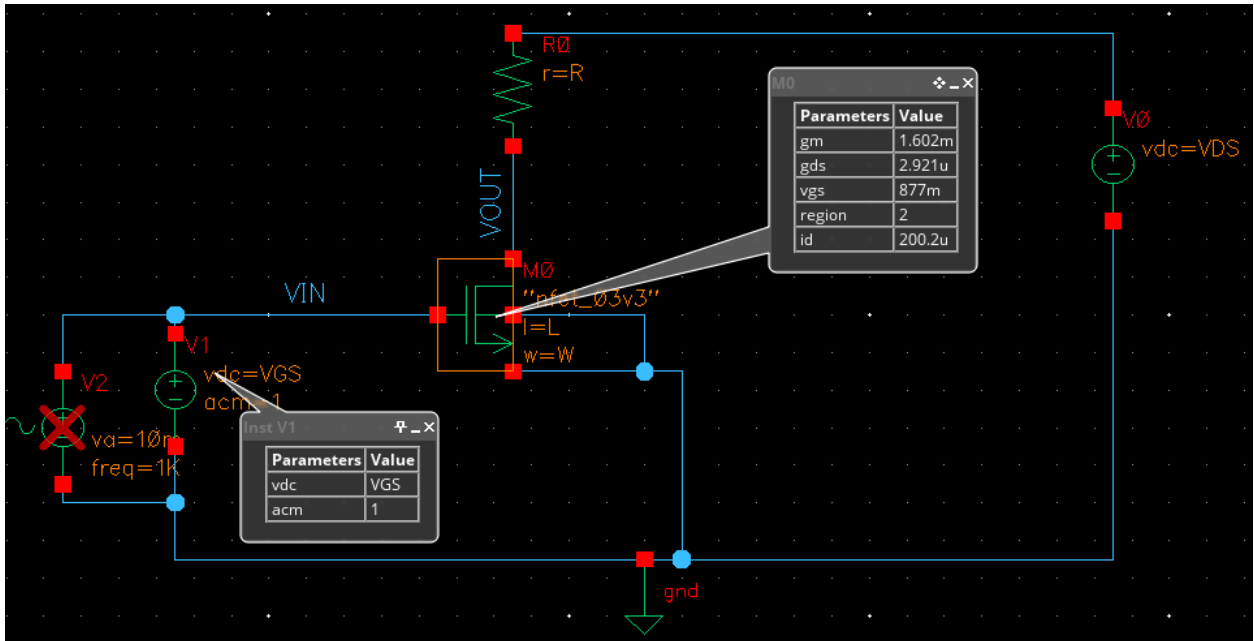

DC OP:

	Values from simulation	Values from part 1
id	200.2 μA	200 μA
gm	1.602mS	1.599 mS
gds	2.921 μS	2.9155 μS
ro	342.3485 K Ω	342.9943 K Ω

Comparison of r_o and RD :

In this case and from shown table, the output resistance r_o is much larger than the drain resistance RD . Since $r_o \gg RD$, its effect on the overall gain is minimal. Therefore, ignoring r_o in the simulation is a valid approximation and does not introduce significant error.

However, if we were to use a minimum-length channel ($L = L_{min}$), the short-channel effects become more pronounced, and r_o decreases significantly. As a result, ignoring r_o in that case could lead to noticeable error in gain calculations. So, the error would not remain the same when using minimum-length devices.

Analytical Calculation of Gain:

| Intrinsic gain | = $g_m \cdot r_o = 548.44 \text{ K}\Omega$ - - - - - | analytic gain | = $g_m \cdot R_d = 12.02 \text{ K}\Omega$

After calculating the analytical gain, we find that it is **much smaller than the intrinsic gain** of the transistor.

This means the relationship is:

Analytical Gain \ll Intrinsic Gain

The intrinsic gain ($g_m \cdot r_o$) represents the maximum theoretical gain of the device, while the analytical gain is limited by external circuit components such as the drain resistance (R_D).

Ask ChatGPT

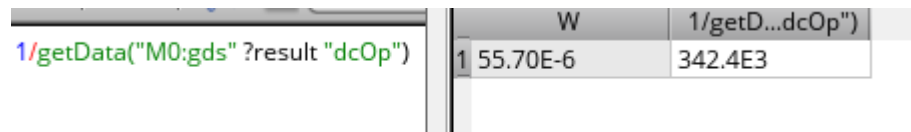


Figure 11: calculate r_o from simulation

Ac simulation:

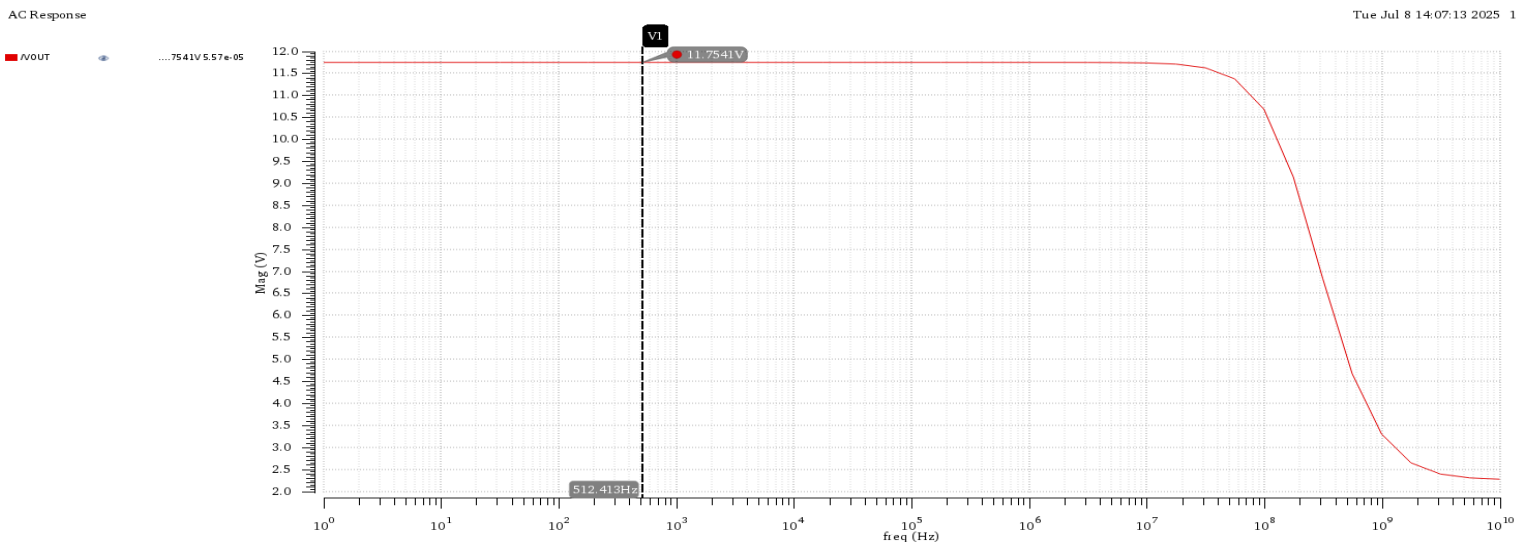


Figure 12: Gain VS freq

Magnitude of DC gain = $11.7541 \approx 12 \text{ V}$

Our design specification requires a minimum DC gain of approximately 12 V. The obtained result is very close to this target, meaning the design meets the specified gain requirement within acceptable margin and approximately satisfy our specs.

Gain non-linearity:

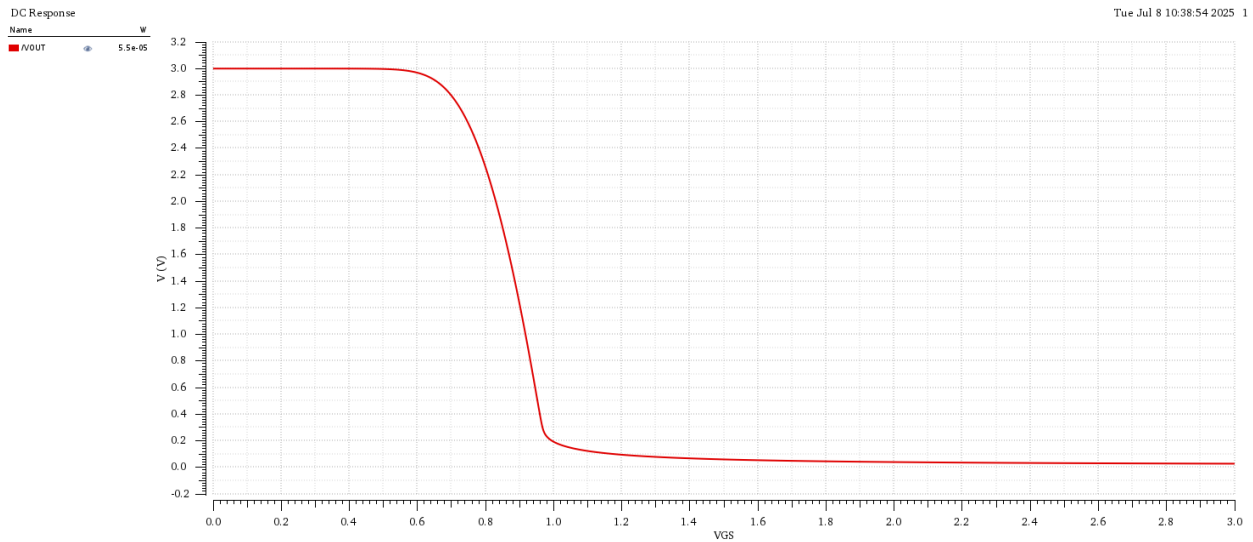


Figure 13: V_{out} vs V_{in}

V_{OUT} vs. V_{IN} Report and Linearity:

The relationship between V_{OUT} and V_{IN} is **non-linear** because V_{OUT} changes significantly at different values of V_{GS} . As the MOSFET moves through the cutoff, triode, and saturation regions, its behavior changes, causing the output voltage to vary in a non-linear manner with respect to the input voltage.


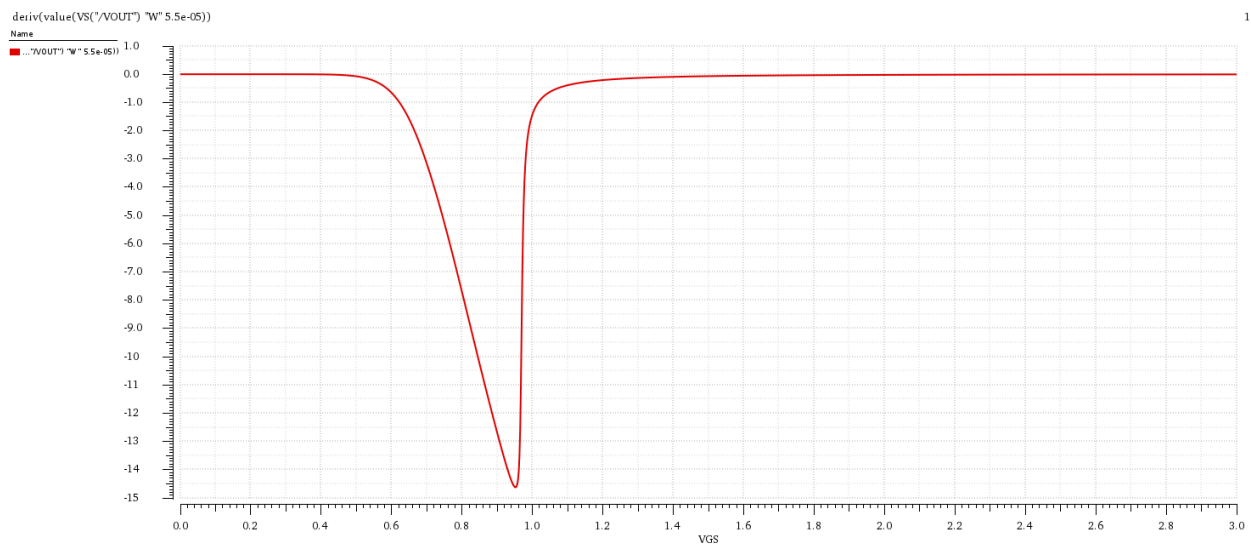


Figure 14: derivative of V_{OUT}

Is the gain linear (independent of the input)? Why?

The gain is **nonlinear**, but at small input voltages (V_{IN}), the gain is approximately linear, though it still depends on V_{IN} to some extent. As the input increases, the transistor transitions through different operating regions, causing the gain to vary and show nonlinear dependence on the input.

Transient analysis :

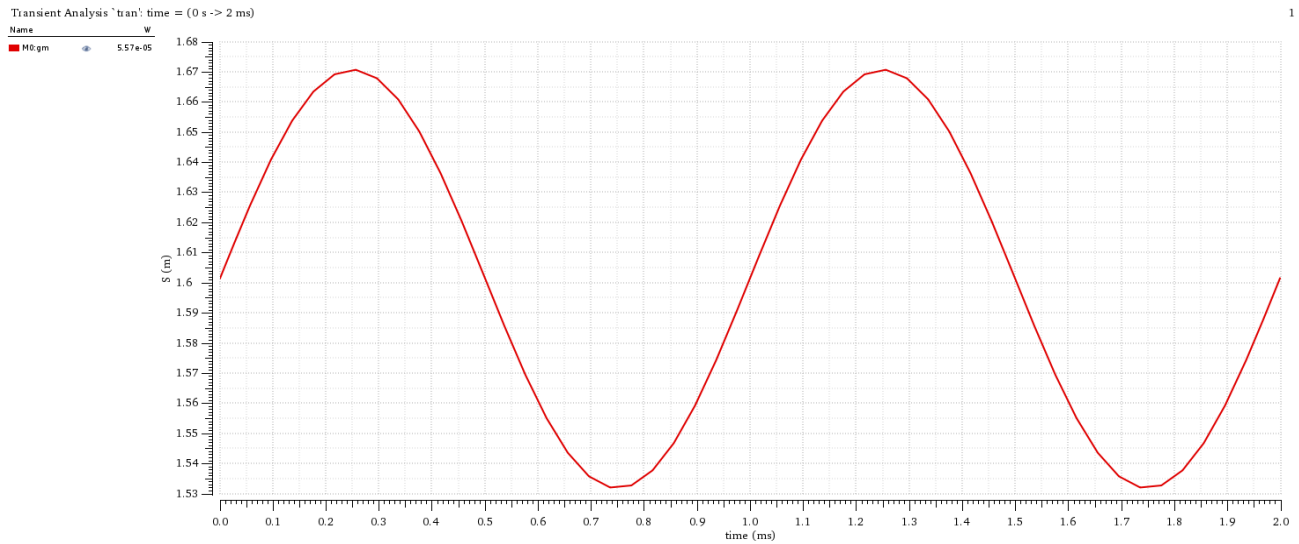

Does gm vary with the input signal?

Based on the time and width (W) data provided, we can infer that gm likely does vary with the input signal since the width values change over time

What does that mean?

The variation in gm with the input signal indicates that the amplifier's transconductance is signal-dependent. This suggests the amplifier is operating in a non-linear region for at least part of the input signal range, as gm would remain constant in a perfectly linear operation.

Is this amplifier linear?

The amplifier appears to be non-linear based on:

- The changing width (W) values over time indicate the operating point is changing with the input signal.
- The variation in gm confirms non-linear behavior