

Analog IC Design (Xschem,Ngspice,ADT0

Lab 03

Cascode Amplifier

Part 1: Device Sizing Using SA

Parameter	Value
$Av = gmro$	50
gm/I_D	10 S/A
Supply (V_{DD})	1.8 V
Quiescent (DC) output voltage	$V_{DD}/2 = 0.9 V$
Bias Current	20 μA

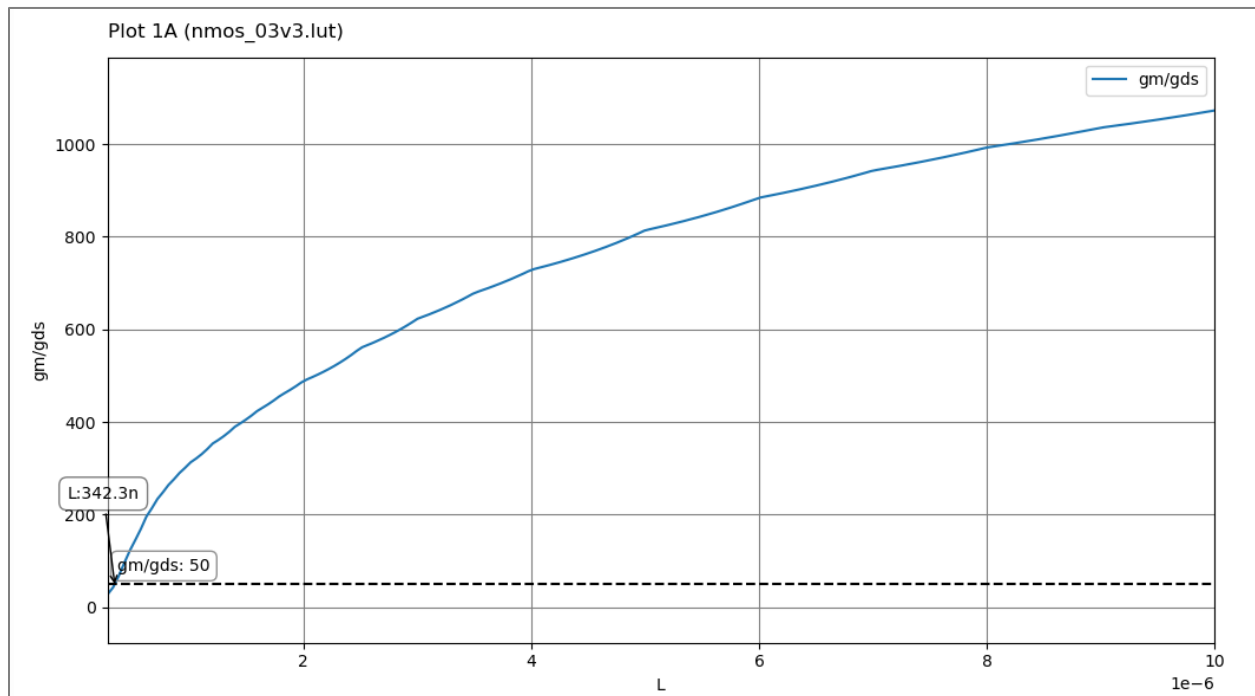


Figure 1: $gm \cdot ro$ VS L

I chose $L = 350 \text{ nm}$ instead of $L = 342.3 \text{ nm}$ to add a margin for process variations and to ensure that $\left(\frac{gm}{g_{ds}}\right)$ remains above 50.

ID ?
 gm/ID ?
 L ?
 VDS ?
 VSB ?
 Stack ?

Results:


Name		TT-27.0
1	ID	20u
2	IG	N/A
3	L	350n
4	W	3.49u

Y-Expr ?

▼

From ADT:

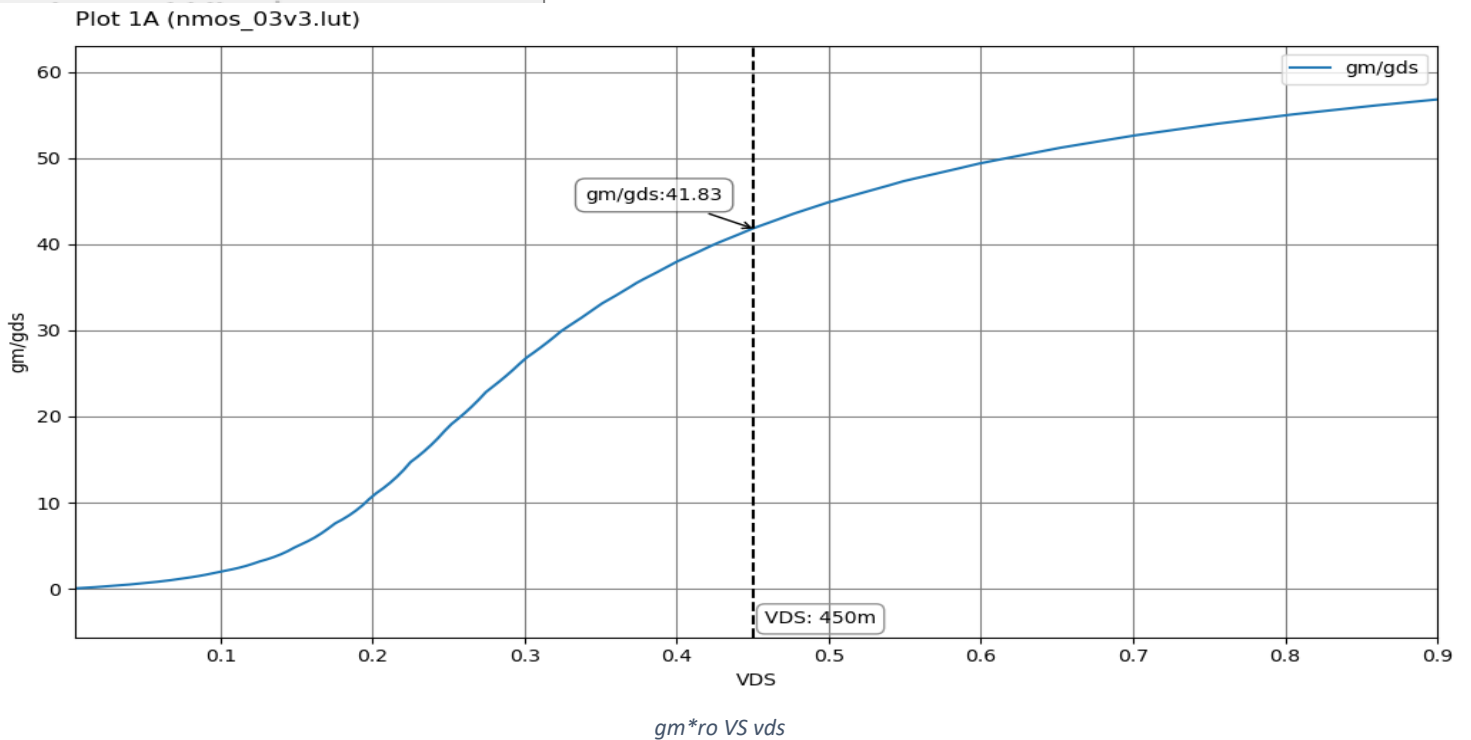after adjusting values for L & VDS & ID & gm/ID
we got W=3.49u




Comment:

AS shown $\left(\frac{g_m}{g_{ds}}\right)$ depends on VDS , where at $v_{ds}=0.45 \rightarrow \left(\frac{g_m}{g_{ds}}\right) = 41.83$

PART 2: Cascode for Gain :

1. OP Analysis :

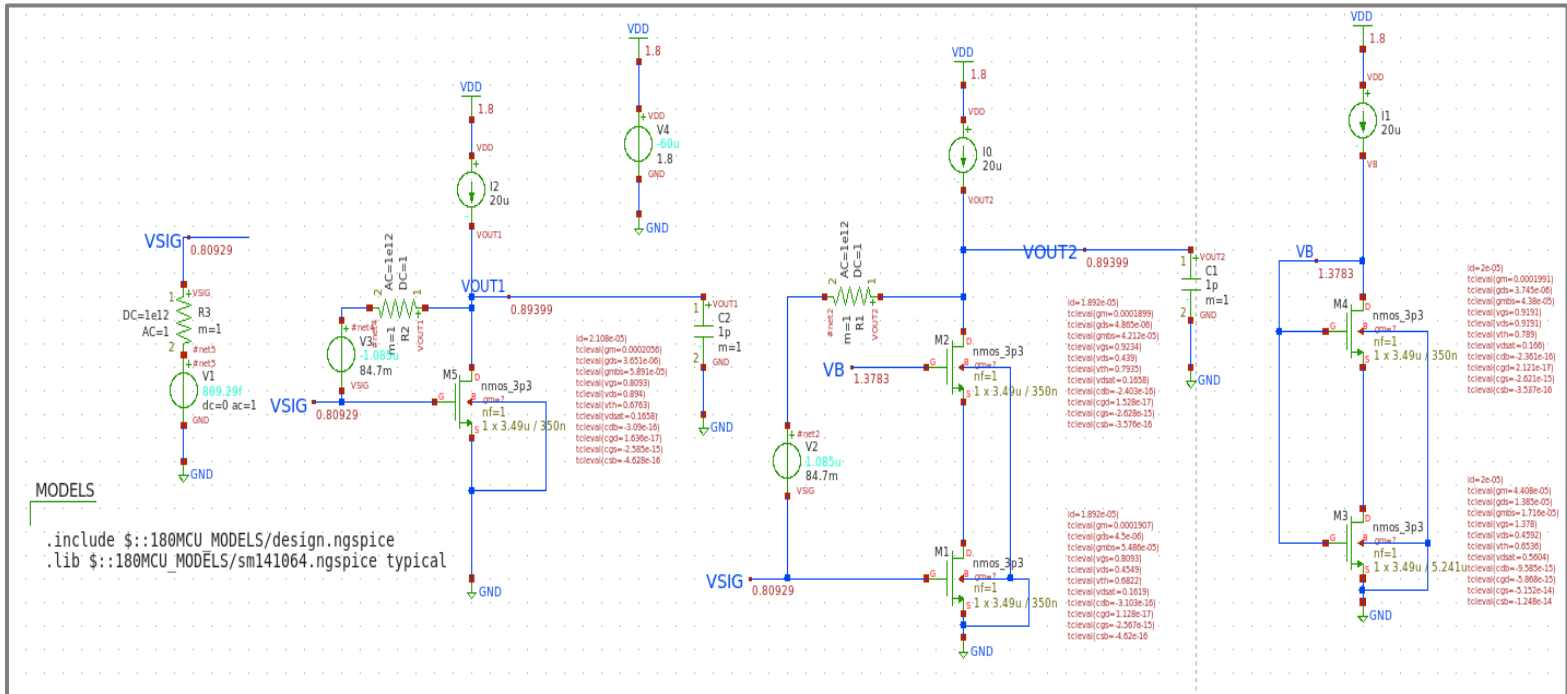


schematic

ID	20u	?
W	3.49u	?
L	350n	?
VDS	0.45	?
VSB	0	?
Stack	1	?
Results:		
Name	TT-27.0	
3 L	350n	
4 W	3.49u	
5 VGS	815.3m	

To calc value of **dc source** we will clac value of VGS5
As shown and the source value will= $0.9-VGS5=84.7mV$

ID	20u	?
W	3.49u	?
L	350n	?
VDS	0.45	?
VSB	0.45	?
Stack	1	?
Results:		
Name	TT-27.0	
3 L	350n	
4 W	3.49u	
5 VGS	928m	

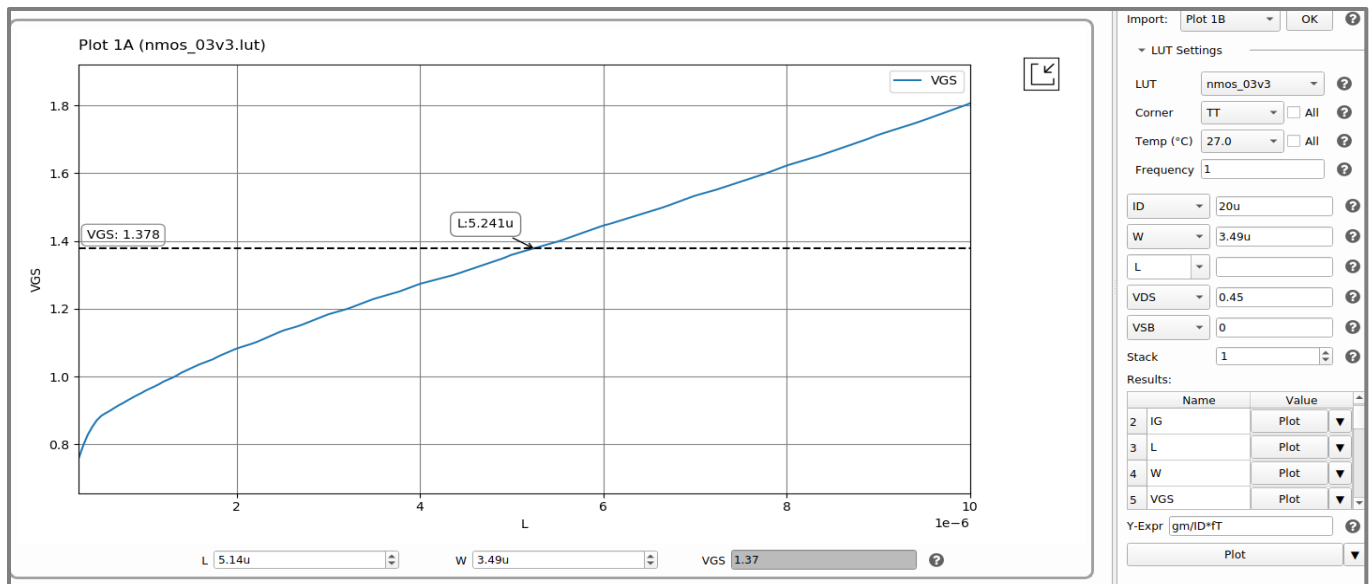To clac value of **VB** we will clac value of VGS2
and VB will = $0.45+VGS2=1.378V$
After that We will use it to calc value of **L3**



As shown $L_3 = 5.241\mu$

10) Check that all transistors operate in saturation. Does any transistor operate in triode? Why?

All transistors operate in saturation except M3, because $V_{dsat3} > V_{ds3}$

11) Do all transistors have the same V_{th} ? Why?

Transistors have not the same V_{th} due to

Body Effect (Substrate Bias)

The threshold voltage depends on the voltage between the source and the substrate (VSB). If the substrate bias varies, V_{th} will also change

Drain-Induced Barrier Lowering (DIBL)

At higher drain-to-source voltages (VDS), the electric field from the drain can lower the potential barrier in the channel, effectively reducing V_{th}

12) What is the relation (\ll , $<$, $=$, $>$, \gg) between g_m and g_{ds} ?

$g_m \gg g_{ds}$ [M0, M1, M2, M4]

$g_m > g_{ds}$ [only M3 (TRIODE)]

What is the relation (\ll , $<$, $=$, $>$, \gg) between g_m and g_{mb} ?

$g_m > g_{mb}$ [M0, M1, M2, M4]

$g_m > g_{mb}$ [only M3 (TRIODE)]

What is the relation (\ll , $<$, $=$, $>$, \gg) between c_{gs} and c_{gd} ?

$C_{gs} \gg c_{gd}$ [M0, M1, M2, M4]

$C_{gs} > c_{gd}$ [only M3 (TRIODE)]

What is the relation (\ll , $<$, $=$, $>$, \gg) between c_{sb} and c_{db} ?

$C_{sb} > c_{db}$ [M0, M1, M2, M4]


$C_{sb} > c_{db}$ [only M3 (TRIODE)]

2. AC Analysis


- 2) Use measure expressions to calculate parameters (DC gain, BW, GBW, and UGF) and export them to a text file.

```
1 max_gain_cs = 5.604095e+01
2 bw_cs = 6.017334e+05
3 gbw_cs = 3.372171e+07
4 ugf_cs = 3.401296e+07
5 max_gain_casc = 2.138377e+03
6 bw_casc = 1.340691e+04
7 gbw_casc = 2.866903e+07
8 ugf_casc = 2.894499e+07
```

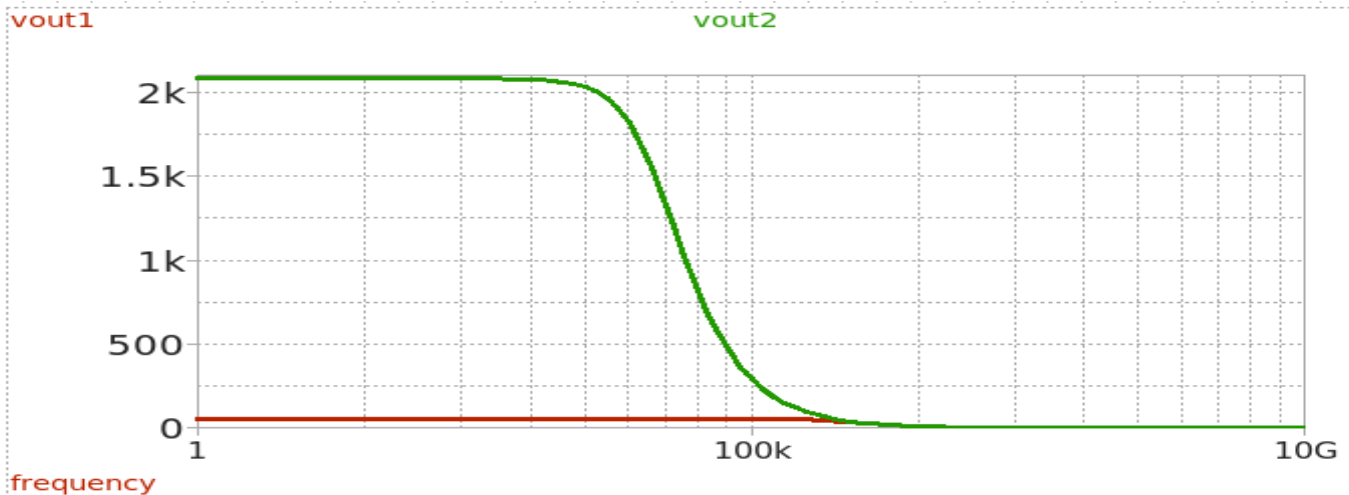- 3) Report the Bode plot (magnitude) of CS and cascode appended on the same plot



VOUT1_VOUT2 VS freq :(linear scale)

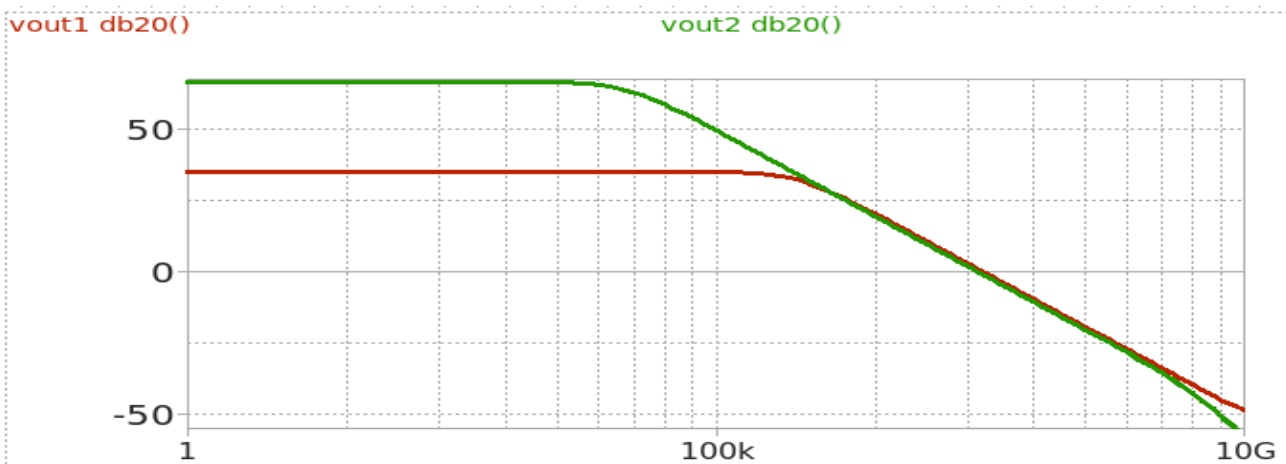

VOUT1_VOUT2 VS freq :(db scale)

Hand analysis:

In a **common source** amplifier , **dc gain** (mag) given by :

$$A_V = g_m \times r_o = g_m \times \frac{1}{g_{ds}} = 56.31$$

But In a **cascode amplifier** , **dc gain** (mag) given by:

$$A_V = g_m \times R_{out} = g_{m1} \times r_{o2}(g_{m2} + g_{mb2})r_{o1} \approx 2.066 \text{ K}$$

In a **common source** amplifier , **(BW)** given by :

$$\frac{1}{2\pi \times r_{o5} \times C_L} = 593.1 \text{ KHZ}$$

But In a **cascode amplifier** , **(BW)** given by:

$$\frac{1}{2\pi \times R_{out} \times C_L} = 14.21 \text{ KHZ}$$

Cs : **GBW** nearly = **UGF** = $BW \times A_v = 33.4 \text{ MHZ}$


Cascode : **GBW** nearly = **UGF** = $BW \times A_v = 29.4 \text{ MHZ}$

	CS	Cascode
DC gain hand analysis	56.31	2.066 K
DC gain from simulation	56.04	2.138 K
BW hand analysis	593.1 KHZ	14.21 KHZ
BW from simualtion	601.7 KHZ	13.41 KHZ
GBW hand analysis	33.4 MHZ	29.4 MHZ
GBW from simulation	33.7 MHZ	28.7 MHZ
UGF hand analysis	33.4 MHZ	29.4 MHZ
UGF from simualtion	34.01 MHZ	28.94 MHZ



COMMENT



The cascode is preferred when high DC gain is critical, while the CS stage is better for wider bandwidth applications. Their GBW remains similar, demonstrating a fundamental trade-off between gain and speed.

Part 3: Cascode for BW

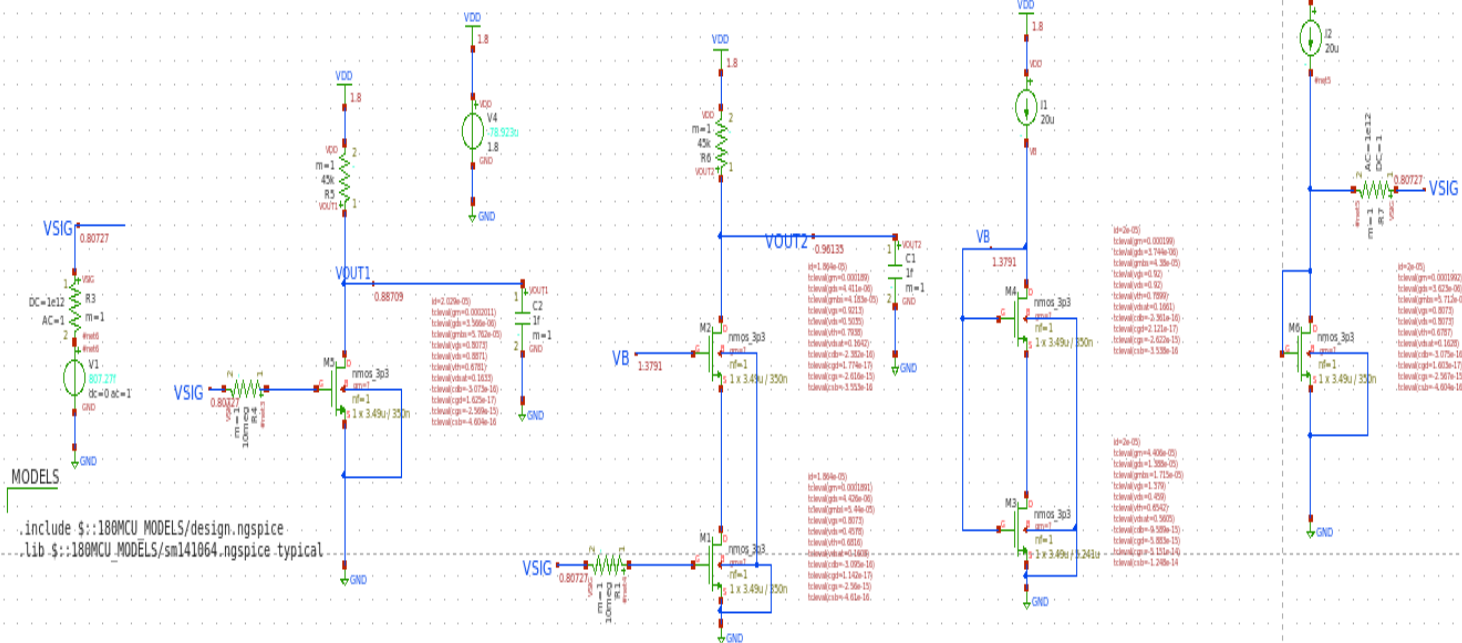

schematic

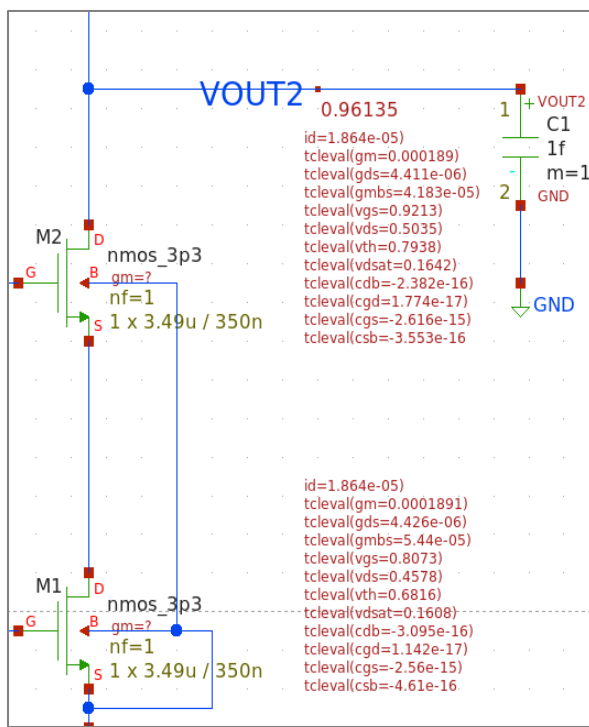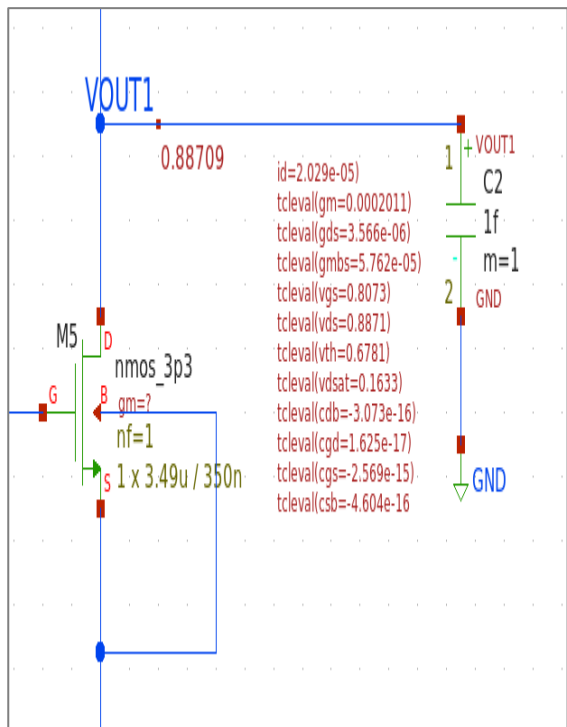

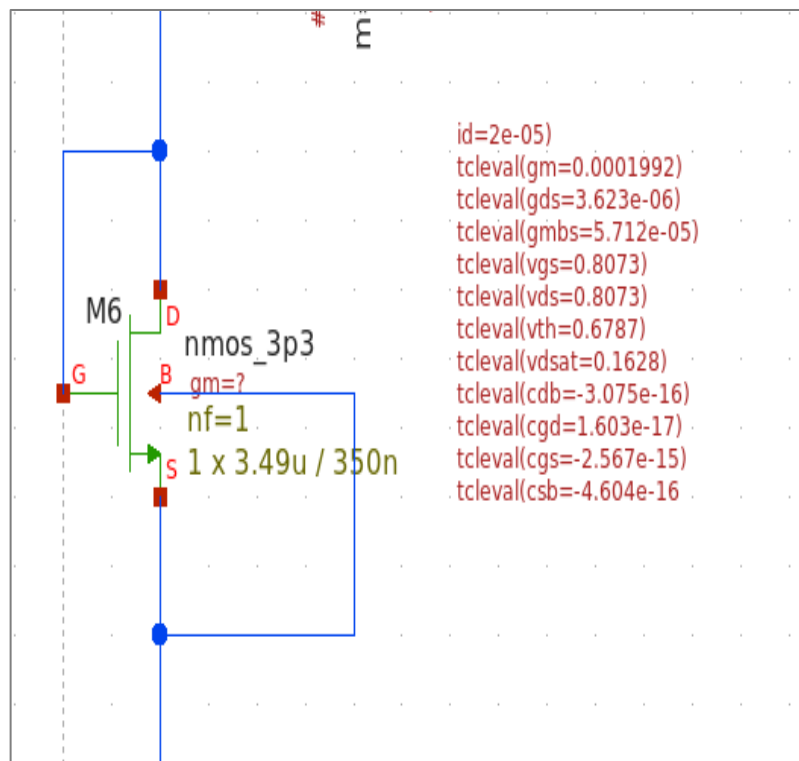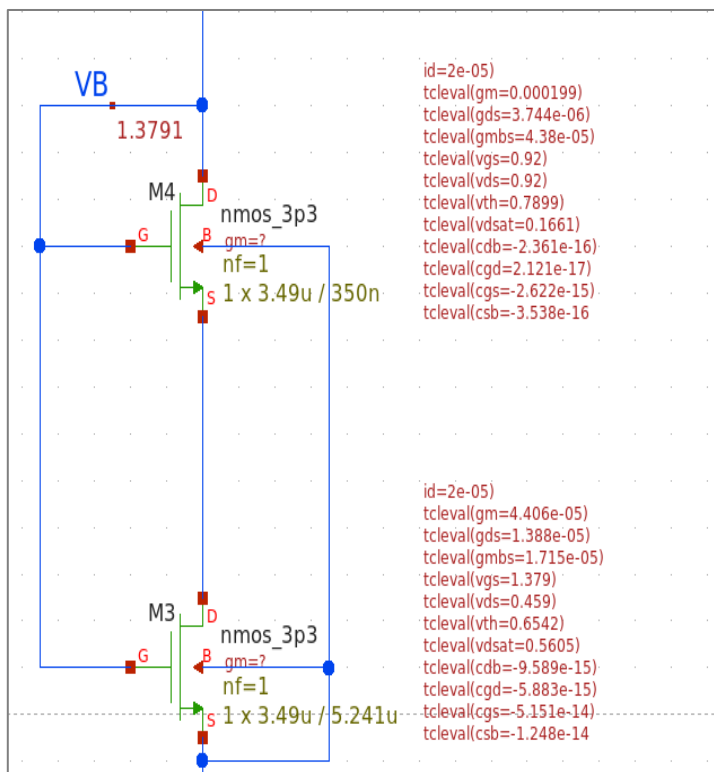

R_D the voltage drop on it is $\approx V_{DD}/2 \longrightarrow R_D = \frac{V_{DD}}{2 \cdot I_D} = 45 \text{ K}\Omega$

4) Check that all transistors operate in saturation. Does any transistor operate in triode? Why?

→ All transistors operate in saturation except M3, because $V_{dsat3} > V_{ds3}$

caps values:

Info: [Sizing Assistant] The resultant point 'CGS = 3.269f'
 Info: [Sizing Assistant] The resultant point 'CGD = 614.2a'
 Info: [Sizing Assistant] The resultant point 'CDB = 2.194f'
 Info: [Sizing Assistant] The resultant point 'CSB = 3.06f'

Caps values for M5

Info: [Sizing Assistant] The resultant point 'CGS = 3.261f'
 Info: [Sizing Assistant] The resultant point 'CGD = 682.2a'
 Info: [Sizing Assistant] The resultant point 'CDB = 2.389f'
 Info: [Sizing Assistant] The resultant point 'CSB = 3.061f'


Caps values for M2

AC Analysis


Use measure expressions to calculate parameters (DC gain, BW, GBW, and UGF) and export them to a text file.

```
1 max_gain_cs = 7.798065e+00
2 bw_cs = 1.700767e+06
3 gbw_cs = 1.326269e+07
4 ugf_cs = 1.321444e+07
5 max_gain_casc = 8.321841e+00
6 bw_casc = 3.016187e+06
7 gbw_casc = 2.510023e+07
8 ugf_casc = 2.489442e+07
```

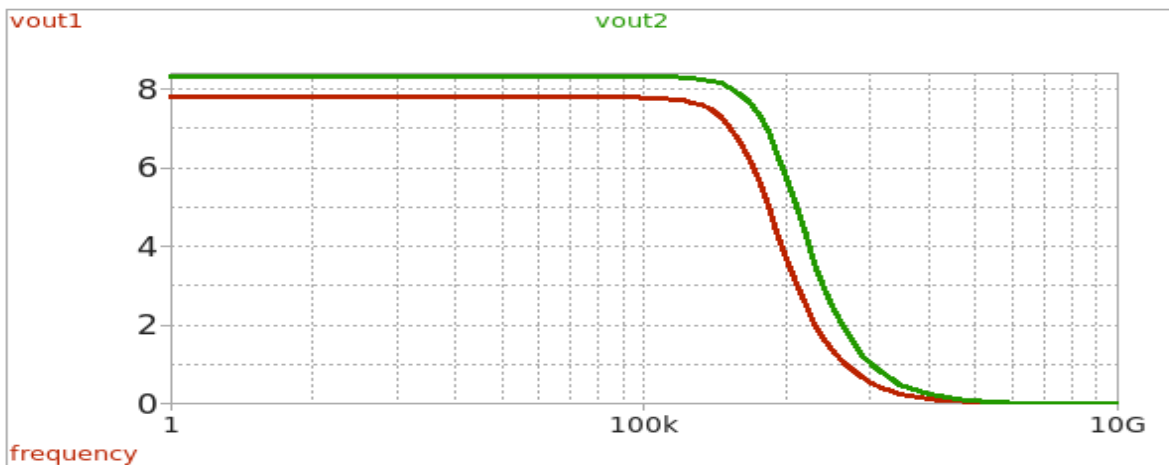Report the Bode plot (magnitude) of CS and cascode appended on the same plot



VOUT1_VOUT2 VS freq :(linear scale)

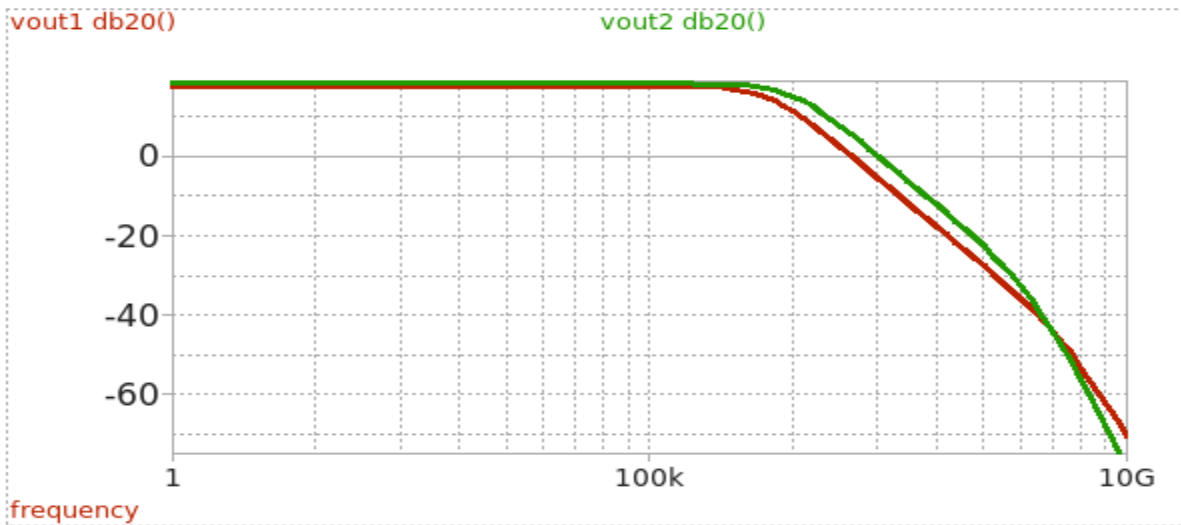

VOUT1_VOUT2 VS freq :(db scale)

Hand analysis:

In a **common source** amplifier , **dc gain** (mag) given by :

$$A_V = g_m \times r_o // R_d = 7.798$$

But In a **cascode amplifier** , **dc gain** (mag) given by:

$$A_V = g_m \times R_{out} = g_{m1} \times r_{o2}(g_{m2} + g_{mb2})r_{o1} \approx 8.48$$

In a **common source** amplifier , **(BW)** given by :

$$\frac{1}{2\pi \times R_{in} \times C_{in}} = \frac{1}{2\pi \times R_{sig} \times (C_{gs} + C_{gd}(1 + A_V))} = 1835 \text{ KHZ}$$

But In a **cascode amplifier** , **(BW)** given by:

$$\frac{1}{2\pi \times R_{in} \times C_{in}} = \frac{1}{2\pi \times R_{sig} \times (C_{gs} + 2C_{gd}(1 + A_V))} = 3441 \text{ KHZ}$$

Cs : GBW nearly = UGF = BW \times Av= 14.31 MHZ

Cascode : GBW nearly = UGF = BW \times Av= 29.18 MHZ

	CS	Cascode
DC gain hand analysis	7.798	8.48
DC gain from simulation	7.798	8.322
BW hand analysis	1835 KHZ	3441 KHZ
BW from simualtion	1700 KHZ	3016 KHZ
GBW hand analysis	14.31 MHZ	29.18 MHZ
GBW from simulation	13.26MHZ	25.1 MHZ
UGF hand analysis	14.31 MHZ	29.18 MHZ
UGF from simualtion	13.21MHZ	24.89 MHZ

COMMENT

The cascode amplifier offers higher bandwidth, slightly higher gain, and nearly double GBW compared to the common source amplifier. This makes it a better choice for high-frequency applications.